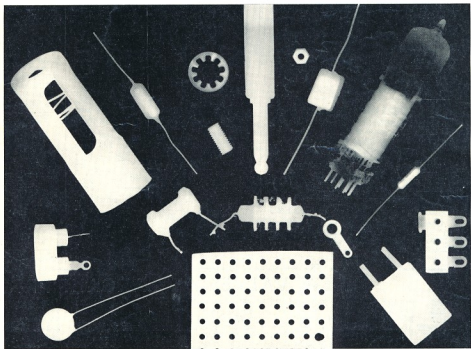


# AMATEUR RADIO

APRIL 1963



Vol. 31, No. 4



2/-

# HAM RADIO SUPPLIERS

5A MELVILLE STREET, HAWTHORN, VICTORIA

Phone 86-6465

North Balwyn tram passes corner. Money Orders and Postal Notes payable North Hawthorn P.O. 5/- Packing Charge.

## SCOTCH BRAND RECORDING TAPE

Brand New, Bankrupt Stock  
on 5 1/2 Reels

1275 feet, 42/-; usual price 62/-.  
850 feet, 30/-; usual price 42/-.

## LSG11 SIGNAL GENERATOR

120 Kc.-390 Mc.  
Freq. range (six  
bands): 120 Kc. to  
130 Mc. on funda-  
mentals; 120 to 390  
Mc. on harmonics.  
Mod. freq. 400 and  
1,000 c.p.s. Tubes:  
12BH7, 6AR5. Rec-  
tifier: half wave  
selenium. Provision  
for crystal oscil-  
lator (not supplied),  
1 to 15 Mc. 100, 117 or  
230v. a.c. input, 50/60 c.p.s. Size: 7 1/2 x 10 1/2 x  
4 1/2 in. Weight: 6 lb.

Price: LSG11—£16/17/6 inc. tax



## CO-AXIAL CABLE

50 ohm, UR67, 3/8" diam., in 25 yd.  
Rolls 30/-; or 1/6 yard.  
52 ohm UR43, 3/16" diam., in 12 yd.  
Rolls 15/-; or 1/6 yard.  
50 ohm UR32, 3/16" diam., in 100 yard  
Rolls £7/10/0.  
72 ohm UR70, 3/16" diam., in 25 yd.  
Rolls 30/-; or 1/6 yard.

## AMERICAN POTENTIOMETERS

American Bradley, 2" long, 1/2" shaft,  
1" diam. Available in following sizes:  
20,000, 25,000, 30,000, 50,000, 100,000,  
250,000 ohms, 1/2, 1 and 2 megohms.

Price 2/6 each

## BARGAINS!

Dial Globes, Madza, 9/- per box of 10  
Dial Globes, 40 mA. .... 1/- ea.  
Egg Insulators ceramic, 1 1/2" & 1", 9d. ea.  
Three-core domestic Cable 2/3 a yard  
Hook-up Wire, 10/010, red, black and  
Green, 4d. yard, or 30/- 100 yd. roll.  
Earphone Inserts No. 2, actuating dia-  
phragm type, ideal as small spkr., 7/6  
Pye dble, bulkhead mtg. Coax Conn., 2/6  
Pye Coax Connectors .... 4/- pair  
English Soax Connectors, plug and  
socket, suit 3/8" cable, .... 4/- pair  
English Coax Connectors, right angles  
to suit .... 4/- each

Crystal Sockets, DC11 .... 2/6 each  
Crystal Sockets, FT243 and min., 2/9 ea.  
Jack Boxes, SCR522 type, cont. 10K pot.  
and knob, 3 1/2" x 1 1/2" x 2" .... 3/6 each  
AR8 Cables 10 ft. long, 8-pin plugs, 10/-  
English Filter Chokes, Pye type, 40-  
mA., 100 ohm .... 3/6  
SCR522 28-volt Genemotor power sup.,  
20/-, 5/- packing

Low Impedance Headphones 12/6 pair  
Carbon Microphones .... 12/6 pair  
Vibrators, Oak/M.S.P., 6 volt, synchron-  
ous, 7-pin AV5211R .... £1  
Octal Plug and Socket, American Am-  
penol, in metal screw case, 8/6 each  
Scope Soldering Irons, to clear 55/-  
Complete with transformers .... £5  
Ceramic Variable Condensers, small, 5  
to 60 pF., Eddystone .... 28/-  
Ceramic 1/2" Shaft Couplings .... 3/6  
Vibrators, 4-pin 6 volt, non-synchron-  
ous, M437 .... 42/-  
Vibrators, 4-pin 12 volt, non-synchron-  
ous, M438 .... 42/-  
Valve Socket and Shield, 9-pin Mc-  
Murdo .... 4/6  
EF50 Valve and Ceramic Socket .... 6/6  
EA50 Valve Sockets .... 1/6

## BARGAINS!

## TECH MULTIMETER



300  $\mu$ A. movement  
AC and DC voltages:  
0-10, 0-50, 0-250, 0-500,  
0-1,000  
Current ranges (mA.):  
0-1, 0-100, 0-500 mA.  
Ohms range: 0-100,000  
ohms.  
Size: 3 1/2 x 2 1/2 x 1 1/2  
inches.  
Complete with leads.

Price only £3/10/0, post paid.

## IN21 SILICON DIODES

U.h.f. mixer, design freq. 3,060 Mc.  
7/6 each, or 3 for £1.

## METERS

0-500  $\mu$ A. (scaled 0-600V., No. 128 Type)  
1 1/2" hole, 1 1/2" round case, new, 30/- ea.  
0-50 mA., 3 1/2" round, 2 1/2" hole, brand  
new .... 30/- ea.  
MR2P 0-1 mA., 1 1/2" square, 35/- inc. tax  
MR52 0-1 mA., 2 1/2" square, £2 inc. tax  
MR65 0-1 mA., 3" square, 47/6 inc. tax  
MO65 0-1 mA., 3 1/2" round, 35/- inc. tax

## CRYSTAL MICROPHONES

Price only

57/6



Stand to suit  
15/- extra.

Model BM3 (illustrated): Response 100-6000 c/s.,  
fitted with 6 ft. cable and phone plug with on-  
off switch. Can be used on stand for hand use.

BM3 Insert .... 10/- each  
Piezo LM3, lapel type .... 25/-  
Piezo HM7, hand type w/plug, 35/-  
Piezo SM1, hand type w/plug, 27/6  
Piezo DX29, Dynamic Mike, pencil type  
with stand, low impedance, £42/6

Call Books 6/-, Log Books 5/6, post ext.

## NEW VALVES AT BARGAIN PRICES

1A3 2/6 10 a £1	3A5 10/-	6K7 5/- 5 a £1	7W7 2/6 10 a £1	6360 £2/10/-	EF70 5/- 5 a £1
1A5 5/- 5 a £1	3A7 25/-	6K8G 20/-	12A6 5/- 6 a £1	717A 7/6 3 a £1	EF72 5/- 5 a £1
1C7 3/- 7 a £1	3BP1 35/-	6K8GT 12/6	12AH7 5/- 5 a £1	807 7/6 3 a £1	EF73 5/- 5 a £1
1D5GT 5/- 5 a £1	5U4GB 14/6	6L7 5/- 5 a £1	12AT7 15/-	808 10/-	EL41 10/-
1D8 7/6 3 a £1	5V4G 15/-	6SA7 7/6	12AU7 15/-	809 20/-	EY31 5/-
1H4 5/- 5 a £1	5Y3GT 13/9	6SC7 7/6	12C8 5/-	815 15/-	KT61 (6V6) 15/-
1H5 5/- 5 a £1	5Z3 17/6	6SP5 7/6 3 a £1	12H6 3/6	820B 15/-	QQE03/12 47/6
1H6 5/- 5 a £1	6A3 7/6 3 a £1	6SH7 4/- 5 a £1	12J5 5/- 5 a £1	832A 19/6	QQE04/20 43/6
1K4 5/- 5 a £1	6AG7 12/6	6SJ7 12/6	12SA7GT 10/-	866 20/-	QQV06/40 97/6
1K5 5/- 5 a £1	6AJ5 7/6 3 a £1	6SN7 12/6	12SC7 5/- 5 a £1	954 5/- 5 a £1	RL18 7/6 3 a £1
1LN5 (CV781)	6AM6 (EF91) 10/-	6S87 7/6 3 a £1	12SK7 5/- 5 a £1	955 5/- 5 a £1	UL41 7/6 3 a £1
5/- 5 a £1	6B7 10/-	6T7 7/6 3 a £1	12SQ7 5/-	956 5/- 5 a £1	VR53 5/- 5 a £1
1M5G 5/- 5 a £1	6BE6 15/-	6V4 11/4	12SR7 5/- 5 a £1	958A 2/6 10 a £1	VR101 5/- 5 a £1
1P5 2/- 10 a £1	6C4 5/- 5 a £1	6V6GT 16/-	14A7 3/6 7 a £1	AV11 2/11	VR102 5/- 5 a £1
1Q5 3/- 5 a £1	6C5 5/- 5 a £1	6X4 10/-	1625 5/- 5 a £1	DL75 2/6 10 a £1	VR103 5/- 5 a £1
1R5 10/-	6C8 10/-	6X5 15/-	1626 5/- 5 a £1	ED50 2/- 10 a £1	VR105 10/-
1T4 5/-	6CH6 2/-	6Y5 5/- 5 a £1	1629 5/- 5 a £1	ECB1/6A 10/-	VR136 2/- 12 a £1
2A5 7/6	6D6 5/- 5 a £1	7A8 2/- 11 a £1	2051 5/-	ECC35 20/-	VR137 2/6
2A6 7/6	6F5 7/6	7C5 5/- 5 a £1	30 1/3	ECH33 20/-	VT25 5/-
2D21 15/-	6F6 12/6	7C7 2/- 12 a £1	35T 30/-	EF36 5/- 5 a £1	VT78 3/6
2X2 5/- 5 a £1	6F8 5/-	7E6 3/6 7 a £1	5763 22/-	EF39 5/- 5 a £1	VT127 4/11 5 a £1
3A4 10/-	6J6 10/-	787 7/6 3 a £1	6146 £3/10/-	EF50 3/6	VT501 7/6 3 a £1

# "AMATEUR RADIO"

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA. FOUNDED 1910.

APRIL 1963  
Vol. 31, No. 4

**Editor:**  
K. M. COCKING ..... VK3ZFQ

**Publications Committee:**  
G. W. Batty (Secretary) ..... VK3AOM  
A. W. Chandler (Circulation) ..... VK3JLC  
S. T. Clark ..... VK3ASC  
R. S. Fisher ..... VK3OM  
R. W. Higginbotham ..... VK3EN  
E. C. Manifold ..... VK3EM

**Advertising Enquiries:**  
C/o. P.O. Box 38, East Melbourne, C2, Vic.  
OR  
Mrs. BELLAIRS, Phone 41-2535, 478 Victoria  
Parade, East Melbourne, C2, Victoria. Hours  
10 a.m. to 3 p.m. only.

**Publishers:**  
VICTORIAN DIVISION W.I.A.,  
Reg. Office: 65a Franklin St., Melbourne, Vic.

**Printers:**  
"RICHMOND CHRONICLE," Phone 42-2419,  
Shakespeare Street, Richmond, E1, Vic.

★

All matters pertaining to "A.R." other  
than editorial, should be addressed to:  
THE EDITOR,  
"AMATEUR RADIO,"  
P.O. BOX 38,  
EAST MELBOURNE, C2, VIC.

Acknowledgments will be sent following  
the Committee meeting on the second Mon-  
day of each month. All Sub-Editors should  
forward their articles to reach "A.R."  
before the 8th of each month. Any item  
received after the Committee meeting will  
be held over until the next month. Publi-  
cation of any item is dependent upon space  
availability, but in general about two  
months may elapse before a technical  
article is published after consideration by  
the Publications Committee.

★

Members of the W.I.A. should refer all  
enquiries regarding delivery of "A.R." direct  
to their Divisional Secretary and not to  
"A.R." direct. Non members of the W.I.A.  
should write to the Victorian Division, C/o  
P.O. Box 38, East Melbourne. Two months'  
notice is required before a change of mail-  
ing address can be effected. Readers should  
note that any change in the address of  
their transmitting station must, by P.M.G.  
regulation, be notified to the P.M.G. in the  
State of residence, in addition "A.R." should  
also be notified. A convenient form  
is provided in the "Call Book".

★

Direct subscription rate is 24/- a year, post  
paid, in advance. Issued monthly on the  
first of the month, January edition excepted.

★

## OUR COVER

This month the photographer has  
arranged a variety of common radio  
components to form our cover de-  
sign. As a matter of interest, how  
many can you identify? All are  
correct scale size. The following  
were used: disc ceramic condenser,  
xtal socket, ventilated valve shield,  
polyester condenser, lock washer,  
iron dust coil core, phone plug,  
metal threaded nut, mica condenser,  
QJE03/12 valve, 1 watt resistor, tag  
strip, FT241 xtal, "Zephyr" board,  
solder lug, r.f. choke and a wire  
wound resistor.

## FEDERAL COMMENT

★

### WHY NOT A NOVICE LICENCE IN AUSTRALIA?

A recent examination of the major Amateur licensing countries in the world indicated that large increases were taking place at an average annual growth rate of approximately 10%. Further inspection revealed that to a large extent this growth was the result of these countries' interest in their youth. Most large Amateur countries like the U.S.A., U.S.S.R., Brazil, Argentina and Japan have made provision for a restricted licence, in relation to power, frequencies, technical knowledge and code speed. These licences are akin to our own proposals for a Novice licence.

It is self-evident that if early training in the electronic field is a requirement to keep abreast with trends overseas, the Australian Government must see the wisdom of the proposals for a Novice licence in our own country. Our many attempts during the past few years to present a plan acceptable to the licensing authorities has met with little success, despite the support of the Armed Services. The repeated submission of the Institute's proposals which are considered to be realistic and in the best interests of the country, have been met with specious reasons why the proposals are not acceptable.

The main basis for rejection seems to have been on the safety aspects involved and the fear that the licensing authorities will be held responsible in the case of electrocution or the like. Yet why should a 10-watt transmitter be any more lethal than a receiver or an audio amplifier? Anyone who has teenage children today well knows that interest in a hobby is the best way of enabling youth to take a pride in something and "find" themselves in a constructive and not destructive field. It is no more difficult or dangerous for the youth of today, with no prior knowledge, to build himself a receiver or audio amplifier than it was in our youth to build a crystal set. Surely, then, this cannot be the real reason given by the authorities for their repeated refusals for a Novice licence.

If administration is a difficulty, this will come in any growing community and must be catered for appropriately. When a boy grows into a man we do not keep him in short pants—he must be given a man-size suit. There may well be other reasons also, but none of the counter arguments given so far appear to be valid enough to deny youth its chance in the rapidly expanding electronic field.

Whatever the official reasons have been in the past, it is high time that the Government and the authorities review the case of the Novice licence in the light of overseas trends, the benefit for youth on the sociological plane and the long-term acquisition, at no cost to themselves, of a pool of highly qualified and competent men in the technological sphere.

FEDERAL EXECUTIVE, W.I.A.

## CONTENTS

Phasing-Filter S.s.b. Generator	2	Sideband Topics:	
Multiband Mobile Antenna Load- ing Coil	6	Modification to High Frequency Filters	19
High Altitude Nuclear Explosion at Johnson Island and Associated Effects on H.F. Signals at Hobart, Tasmania	7	Using the 5 Mc. Filter	19
Fools' Modulation	8	Mechanical Filters	19
Further Modifications to the No. 122 Transceiver	8	Going to Auckland in June	20
An Effective Noise Silencer	9	VK3 Receiver Fund	20
Heterodyne Frequency Meter with Crystal Calibrator	13	For Beginners: Hearing the Good Ones	21
P.A.C.C. Contest, 1963	20	Federal and Divisional Monthly News Reports	26
Did It Work?	20	Correspondence	20
		DX	23
		SWL	24
		VHF	25

# Phasing-Filter S.S.B. Generator\*

## Dual System for Better Sideband Suppression

DR. LEO H. McMAHON,† VK2AC

SINCE the introduction of Amateur s.s.b. in its present-day form, late in 1947, the two systems of sideband generation—filter and phasing—have been subjected to much experimentation and practical testing. As to a preference between the two methods, the trend toward the filter system, in one form or another, by manufacturers of Amateur equipment may be taken as a guide. This also follows a long-established practice in commercial communications systems. For the home constructor, however, both systems present problems. In the case of the filter system, the main ones are cost, positioning of the basic frequency in respect to the filter response, and sideband switching. With the phasing system, they are in the adjustment of the phasing controls (particularly in r.f. phasing), limitation of the suppression obtainable in practice, and wide frequency response unless special steps are taken to minimise it.

It was considered that if the two systems were combined each in a simple form, the end result would be an improvement, even if each system was not adjusted to a highly accurate degree. The chance to put this into practice came with the availability of a "Sideband Package"<sup>2</sup> built in its originally described form, but in which the sideband generator was not considered satisfactory. This generator was simply replaced by a new one consisting of a low-frequency phasing-type generator, followed by a single half-lattice filter. The end results from this generator have been excellent as to both carrier and sideband suppression.

### AUDIO PHASING CIRCUIT


The phasing system used (see Fig. 1) is essentially the one described by W2EWL,<sup>3</sup> but scaled down to approximately 440 Kc. This frequency was chosen chiefly because suitable crystals were on hand. The exact frequency can be a matter of choice. The audio output at T301 in the original "Package" circuit was found to be sufficient with a little to spare.

There is one minor modification in the input resistor of the B. & W. audio phase-shift network used in the W2EWL circuit. The division of audio voltage input to the network must be in the ratio of 7:2. This ratio is determined by the position of the moving arm of the 500 ohm input potentiometer. However, it is possible to get this ratio in respect to either end of the potentiometer. This may cause confusion which can be avoided by using a fixed 500 ohm resistor as part of the network,

● By combining the features of the phasing and filter types of carrier and sideband suppression, VK2AC finds that more complete suppression is obtainable in practice with less critical adjustment of either section.

so that the higher voltage is always applied to Pins 1 and 5 of the p.s.n. as required. Increasing the total input resistance to 1,000 ohms has little effect in practice. If a potentiometer of less resistance is available, this can be used with a smaller fixed resistance to maintain the total of 500 ohms, if desired.

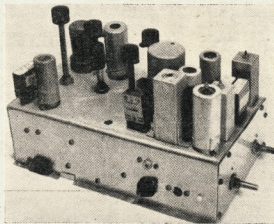The coupling transformers used between the audio phase-shift stage and the balanced modulators are simply a pair of high to low impedance audio transformers. In the original W2EWL unit, it was suggested that 20,000 to 200 ohms be used. Anything of this general nature is satisfactory provided that the two transformers are similar.



### R.F. PHASING

The r.f. oscillator that generates the basic 440 Kc. signal (also shown in Fig. 1) is patterned after the low frequency circuit used in the "Package". The phasing arrangement is a very simple RC network suggested by ZL1AAX.<sup>4</sup> It is coupled to the output tank of the cathode follower. A value of 100 ohms was used for the resistance arm, and the capacitance required for a reactance of this same value is approximately 3,600 pF. Several capacitors of smaller values in parallel are used to make up a total of approximately the required value. Likewise, R3 is

made up of several higher-resistance values in parallel. The resultant capacitance and resistance are juggled until the r.f. voltages measured across the two arms are equal. Once this condition has been attained, no further adjustment of the phasing should be required—a point that should appeal to all who have tried to adjust the two-coil system.

L3 should be a coil of i.f. type that will resonate at 440 Kc. with a capacitance of 100 pF. So far as the coupling coil L4 is concerned, it is necessary that it be only large enough to produce about 2 volts of r.f. peak to peak, across the output terminals. There is no point in making the coil larger than this.

### BALANCED MODULATOR

The balanced modulator is a 440 Kc. version of W2EWL's, using semi-conductors instead of the vacuum diodes. To maintain the same LC ratio in the output circuit requires an increase in capacitance of about 20 times that used at 9 Mc., or a value of 0.02  $\mu$ F. for

VK2AC's sideband generator is constructed to fit in the space occupied by the original generator in the W2EWL exciter. To the left are Y1 and V1, the audio ratio and balance controls, the plug-in p.s.n., and the 12AT7. Near the centre are R1 and R2, the s.b. selector crystals (disregard the frequency marking on the foremost holder), and a round shield can containing L1, L2. In the adjacent line are L3, L4, the 12AU7, and the 6AG5. C2 (hidden) is mounted between the two tubes. At the right-hand end of the chassis are the 6BU6, T2, the filter crystals, and T1.

each of the two capacitors, the resultant of the two in series making a capacitance of 0.01  $\mu$ F. across the coil. (As a convenient way of arriving at the size of coil needed to resonate at 440 Kc. a coil was wound that would resonate at 4,400 Kc. with 1/100 of the capacitance, or 100 pF.) A crude attempt was made to match the 0.02  $\mu$ F. capacitors by connecting them across an audio oscillator and measuring the voltage drop across individual capacitors until a pair with essentially the same drop was found.

Wire wound controls were used at R1 and R2 because they were found to be more reliable and positive in their action than carbon units.

\* Reprinted from "QST," October, 1962.

† 22 Pitt St., Randwick, N.S.W.

<sup>2</sup> Bigler, "A Sideband Package," "QST," June, 1958.

<sup>3</sup> Vitale, "Cheap and Easy S.S.B.," "QST," March, 1956.

<sup>4</sup> Earnshaw, "An Improved Phase Shift System," "CQ," November, 1959.



CRYSTAL FILTER

The output of the balanced modulator feeds a conventional Class A amplifier stage (see Fig. 2) which is followed by a single half-lattice filter. It is possible to overdrive the 6AG5, so the input coupling should be adjusted to avoid this.

The use of a single half-lattice filter in this combination gives all the results required. Surplus crystals were used and, since it is a difficult job for most Amateurs to alter the frequency, a different approach was used in selecting the basic frequency in respect to the filter curve. A study of the surplus crystal frequencies available, shown in

between the two filter-network crystals was sufficient. This represents the difference between Channels 320 and 319. Then, depending on the type of microphone in use and the general pitch of the operator's voice, the carrier frequency chosen was 463 or 1389 cycles below the lower-frequency filter crystal. The carrier crystal frequency in Fig. 1 is shown as 441.666 Kc.

This procedure is so simple, and gives such good results, that it is advisable to purchase a few odd crystals with which to experiment. The aid of other Amateurs should be enlisted and their opinions sought and studied to decide which carrier frequency is the most

tried in the experimental model but were not found necessary. C3 was made by twisting together two pieces of insulated wire.

SIDE-BAND SELECTION

Sideband selection is accomplished by shifting the frequency of the oscillator feeding the balanced mixer. The system of selection used in the original "Package" was ingenious, but it may give rise to a possible source of trouble. In the frequency-multiplying stages any generation of a fifth harmonic might be applied to later stages and appear as carrier. It is not possible to balance out this fifth harmonic and so the practical carrier suppression may not be satisfactory. Some fifth harmonic energy is always generated in the multiplying stages and can feed into the output stage by devious routes. With the cheapness and availability of crystals ground to a desired frequency, the method shown in Fig. 2 is an easy way to avoid this possible difficulty. The two crystal frequencies should be spaced twice the carrier frequency. Crystals ground to specified frequencies may be obtained reasonably from several firms advertising in "A.R."

CONSTRUCTION

Physically, the unit was constructed to replace the original generator in the "Package". However, a 5" x 9 1/2" x 3" chassis was used to allow mounting of some of the components underneath. The first things mounted were the carrier-insertion potentiometer and the sideband switch to fit in exactly the places occupied by these controls in the original unit. From then on, parts were mounted with an attempt to keep r.f. sections as well spaced and isolated as possible to avoid unintentional coupling. The audio transformers were mounted underneath on opposite sides of the chassis. The diodes were mounted between the balancing potentiometers and the 0.02  $\mu$ F. capacitors, as well spaced as possible and at right angles.

The balanced modulator coil, L1, was mounted above the chassis and covered with a shield, while the Class A input coil, L6, was mounted underneath.

ADJUSTMENT

In the adjustment of any s.s.b. transmitter, the use of a v.t.v.m. with an r.f. probe is almost mandatory. The first step in the adjustment is to see that the two crystal oscillators are operating properly. In the lower-frequency oscillator, the input to the arm of each balance potentiometer is about 2 volts peak to peak. This is not a very large value, but it is quite sufficient for the purpose.

The next step is to peak all of the tuned circuits. To do this, the crystals are removed from the filter, and one of them put in the oscillator. A spare FT-243 crystal, or a capacitor of about 10 pF., is inserted in one of the filter sockets to provide a small amount of capacitive coupling across the filter.

Set the phasing capacitor, C2 to minimum, and unbalance the modulator

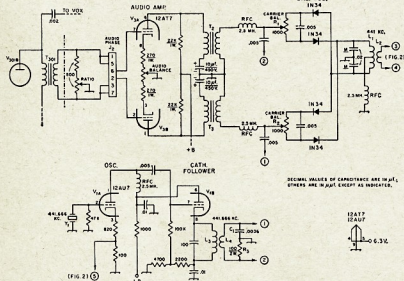


Fig. 1.—Audio and r.f. phasing circuits. Audio output from T301 in the "S.S.B. Package" now goes to the WZEWL phase-shift circuit (portion between broken line in which original component designations are used) instead of to the balanced modulator. R.f. input to the WZEWL balanced modulator is now at 440 Kc. instead of 9 Mc. Semiconductors replace vacuum diodes in WZEWL's balanced modulator. The oscillator circuit is a modification of one used in the "Package". Resistances are in ohms, and fixed resistors are 1/2 watt unless indicated otherwise. M indicates mica. Other fixed capacitors not listed below are disc ceramic. Values in the WZEWL portion of the circuit are the same as in the original.

- C1—Mica capacitors in parallel (see text).
- L1—40 turns No. 24 enamelled, 3/8 inch diam., close wound.
- L2—13 turns wound over centre of L1.
- L3—Approx. 1.3 mH. (see text).
- L4—25 turns wound at ground end of L3.
- R1, R2—Wire wound control.
- R3—Nominal value (see text).
- Y1—Channel 318 (surplus).

the following table,<sup>5</sup> will reveal recurring frequency differences of 1389, 463, 926, 463 and 1389 cycles when two-digit and three-digit channel numbers are interposed.

Channel No.	Fundamental Freq. (Kc.)	Difference Cycles
317	440.277	
38	440.740	463
318	441.666	926
39	442.592	926
319	443.055	463
40	444.444	1389
320	444.444	0
321	445.286	1389
41	445.633	463
322	447.224	926
42	448.148	926
323	448.611	463

By experimenting it was found that a frequency separation of 1389 cycles

satisfactory from an audio point of view in each particular case. This may not seem to be a very scientific approach to the problem, but it represents by far the most satisfactory method from the practical angle.

A variable phasing capacitor (C2) is necessary for adjusting the filter to optimum. To provide a range of adjustment, a small fixed capacitance in the vicinity of 2 to 5 pF. is placed across the lower-frequency crystal, and a small variable capacitor of about 3 to 12 pF. or so across the other.

The transformers used in the filter are of the ordinary type, padded to approximately 440 Kc. and provided with a capacitive centre tap.

BALANCED MIXER

The balanced mixer stage (Fig. 2) uses a 6BU8, which has worked very well and gives a conversion gain of about five. Balancing controls were

<sup>5</sup> This was not definitely confirmed by the author, nor has this difficulty been reported by anyone who has built the "Package". Adequate shielding of the multiplier stages is important, of course.—Editor "QST."

## GRID DIP OSCILLATORS

### FULLY WIRED AND TESTED

Well known American brand EICO. These instruments are exceptionally versatile, stable, rugged and compact units especially suited to the Amateur's and Electronic Serviceman's needs. Easy to hold and thumb-tune with one hand.

Frequency Range: 400 Kc. to 250 Mc. in eight overlapping ranges. **Coils:** Precision factory wound on polystyrene formers; coils are specially treated to prevent the windings from moving if accidentally knocked, etc. **Meter Movement:** 500 microamperes. **Frequency Indication** is by means of a rotating drum (housed inside the case) with 340° rotation; scale length is 3½" long. **Circuit** uses Colpitts type oscillator with improved grid current stability over the tuning range. **Tuning:** Tuning condenser is equipped with a 1:7 ratio planetary drive. **Power Supply:** Self contained transformer operated selenium rectifier. **Dimensions:** 2½" high, 2½" wide, 6½" long.

**PRICE £29/17/8 complete, including Sales Tax**

All goods sent by Certified Post. Be sure to include your **FULL ADDRESS** and Money Order or Cheque with your Order. Easy interest-free terms available if required. **Available from:—**

Phone 40-7844

**THE RADIO EXCHANGE CO.**

Phone 40-9604

**SHOP 1A, ALLAMBIE HEIGHTS SHOPPING CENTRE, ALLAMBIE HEIGHTS, N.S.W.**

Country Clients, Please Note After Hours: XM 7691, XJ 6596

## 500 Kc. PRECISION CRYSTAL OSCILLATORS

Made by American R.C.A. These units are capable of an accuracy of 0.0012%. They are completely contained in a chromed metal case, 4½" high x 1½" wide x 1" deep and consist of a precision 500 Kc. Crystal in a **CRYSTAL OVEN**, a miniature pentode, etc. The unit plugs into a standard 7-pin miniature socket (supplied). Four connections are required, 75-100v. at 2 mA. B+, 6.3v. at 300 mA. fil. and oven heater, earth, and oscillator outut. Complete circuit and details supplied.

**Full Price £6/3/0 including Sales Tax**

All goods despatched by Certified Mail. Be sure to include your full address and cheque or money order with your order.

PHONE OR MAIL ORDERS ONLY

NO CALLERS PLEASE

PHONE: XJ 6181, XJ 2353

## AIR WOUND COILS

### "AIR DUX"

Made by Illumitronic Engineering Corp., Calif.

The Coils designed for Amateurs to give that professionally-built appearance to all equipment.

A full range of 55 different Coils, ranging from ½" to 3" diameter, from 32 to 4 turns per inch, in wire sizes from 10 to 24 gauge, are carried in stock.

**Impedance Matching Baluns** for transmitters and receivers, **500 Watt Silver Plated Pi-Couplers**, **Indented and Variable Pitch Coils** are also available from stock.

**FREE!**

Eight-page illustrated Catalogue, containing technical data, graphs and charts how to design the correct pi-coupler for your transmitter, are available on request.

## WORLD MAPS AND ATLAS

Designed specifically for Radio Amateurs

LATEST EDITIONS

**THE MAP OF THE WORLD** is 42" x 29" and shows: (1) the international Amateur prefixes, (2) Zone Boundaries, (3) Continental Boundaries, (4) Two lists on the bottom of the Map show Countries and Prefixes in alphabetical order for quick reference. Ideal for mounting on the wall of the shack.

25/- plus 1/3 postage.

**THE WORLD ATLAS** is a 12" x 9" book of multi-coloured easy-to-read Maps of Europe, Asia, North America, South America, West Indies, Australia and Pacific Ocean, World Polar projection. All Maps show, in detail, Zones, Boundaries, Principal Towns, Lists of Countries and Prefixes, etc. A must for the operating desk of every Amateur and S.w.l.

25/- plus 1/3 postage.

## TRANSTRONIC PRODUCTS

123 BALGOWLAH ROAD, FAIRLIGHT, N.S.W.

by running one of the balancing potentiometers to one end. With the output stage of the exciter feeding a dummy load, and with some sort of output indicator, such as a v.t.v.m., connected across the load (or a receiver tuned to some output frequency of the transmitter, as described in the s.s.b. chapter of the A.R.R.L. Handbook), all tuned circuits are peaked.

Next, adjust the injection from the crystal oscillator to give maximum gain in the conversion stage. With S1 set to the low frequency crystal, set C5 near maximum capacitance and adjust L7 for maximum injection. Then adjust C3 for optimum injection. Now turn S1 to the high frequency crystal and adjust C4 for the same injection. If the same injection cannot be obtained, it may be necessary to repeat the process with C5 set to a lower or higher value. Optimum injection is a matter of only a few volts. Since this oscillator feeds into a high impedance load, it is easy to overdrive the mixer. As a matter of fact, care must be used constantly to avoid overdriving at any point in the system. Overdriving is a most common fault in many s.s.b. transmitters. It is always better to underdrive than overdrive, so always set the levels a little on the conservative side.


The next step is to see that the circuitry associated with the filter is functioning properly. To do this, remove the FT-243 crystal (or capacitor), and leave the two filter sockets empty. Now vary the phasing capacitor to see if the signal fed through to the output passes through a minimum. It is necessary to find this minimum so that in the final adjustment the capacitor can be set correctly for the most symmetrical response. The null point represents the point at which the circuit is neutralized. This point will be very close to the final correct position. Whatever signal that passes through after the null has been obtained is fed around the filter through stray paths. With the combination of phasing and filtering, a small amount of stray signal is of no importance.

The balanced modulator should now be checked for carrier feed-around. This subject is seldom given sufficient consideration. To make this check, replace the 10 pF. capacitor in one of the filter sockets and then disconnect the two r.f. leads from the balancing potentiometers of the modulator. Put the 441.666 Kc. crystal in the oscillator and then listen on a receiver to one of the transmitter output frequencies. Any signal heard is a result of leak-around and must be minimised.

although they were many inches apart. Shielding of both tubes is necessary. Time spent in getting rid of this leak-around will give you a much better signal.

Now the r.f. leads to the balancing controls can be replaced and the carrier balance controls adjusted for maximum suppression. The greater part of the carrier suppression takes place in the balanced modulator with a little additional help from the filter. (The main contribution of the filter is in elimin-

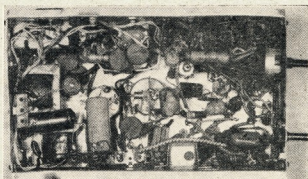Bottom view of the filter/phasing side-band generator. The audio output transformers are mounted at right angles to the left. L5-L6 is mounted against the lower side of the chassis. The balanced modulator diodes are at the centre. Shafts extending to the right are R5 (above) and R1 (below).



Shielded wiring should be used in all power circuits. Remember that a capacitance that makes a good bypass at 9 Mc. may not be sufficient at 440 Kc. The voltage picked up at the cathode of the 441.666 Kc. oscillator should be the minimum required to give full carrier reinjection, since it was found that there was quite a large amount of leak-around directly from the oscillator to the 6BU8 stage. The voltage required at injection grids of the 6BU8 is only on the order of 300 millivolts, peak to peak.

It was found necessary to shield the balanced modulator output coil. After all other steps had been taken to minimise the leak-around, it was found that there was still slight leakage between the oscillator and mixer tubes,

ating the unwanted sideband.) Even without the filter, the residual carrier should be well down in the hum or noise. The stability of carrier suppression of this high degree is quite good, but not absolute.

The next step is to set the sideband suppression controls. This is done first for the phasing system, with crystals removed from the filter and the 10 pF. capacitor substituted as described earlier. By far the easiest and fastest way to set the ratio and audio balance controls is to feed in a single tone of about 1,000 cycles and adjust for minimum response on the unwanted sideband, using a receiver of sufficient selectivity; otherwise, you will have to make use of an oscilloscope pattern. When the audio phasing controls have been set, replace the filter crystals and set the filter phasing capacitor, C2, for maximum sideband suppression. It is in this step that you will need some sensitive detecting device, since the degree of sideband suppression will test the capabilities of any receiver. It gets to a point where it is hard to decide which to believe—the receiver or the generator.

An important point to watch in these adjustments for sideband suppression is to be sure that the same sideband is suppressed in both the phasing system and in the filter. If it becomes evident that opposite sidebands are being suppressed in the two sections, this can be corrected by reversing one set of audio output leads, or the r.f. input leads to the balanced modulator. The setting of the filter phasing capacitor for maximum suppression should come very close to the previous setting made for balance in the crystal filter. Once the suppression controls have been set, the tuned circuits can be rechecked. In all of these adjustments, it is very essential to be sure that no stage is overloaded, since this may lead to false indications.

(Continued on Page 19)

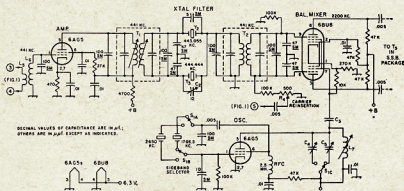


Fig. 2—Crystal sideband filter, balanced-mixer and sideband-selector circuits. This section fits between the balanced modulator of Fig. 1 and the 3.250 Kc. mixer of the "Sideband Package" circuit. The sideband selector replaces the original system in the "Package". Resistances are in ohms, and fixed resistors are  $\frac{1}{2}$  watt unless indicated otherwise. SM indicates silver-mica capacitors not listed below are disc ceramic.

- C1—33-12 pF. trimmer.
- C2—"Gimmick" (see text).
- C3—83-340 pF. trimmer.
- C5—100-500 pF. trimmer.
- L5—5 turns over ground end of L6.
- L6—Same as L3 (Fig. 1).
- L7—20 pF. iron-slug coil.
- R4—Wire wound control.
- S1—Three-pole, two-position rotary switch.
- T1, T2—455 Kc. i.f. transformers.
- Y2—Channel 31B (surplus).
- Y3—Channel 320 (surplus).



# Multiband Mobile Antenna Loading Coil\*

E. ZIEMENDORF, W2IGI, and J. LAMPUS, W2KJV

**T**o most mobile Hams the antenna system presents certain limitations and problems. Multiband operation multiplies the difficulties in nearly direct proportion to the number of bands used. Some of the problems have been overcome over the years by experimentation and "home-brewing," and it is the purpose of this article to describe the results of a recent effort to improve on multiband mobile antennae. Specifically, the article describes the details of construction of a tunable mobile loading coil for the bands from 75 to 10 metres.

The construction of the coil will present no problem to the Ham having access to a small machine shop. Because each Ham may have other sizes and dimensions of material available than those shown in the cutaway view, Fig. 1, drawings and dimensions of the individual pieces will not be shown.

The body of the loading coil is a paper-laminate phenolic tube (Spaulding Fiber)  $1\frac{1}{2}$ " o.d. by  $\frac{1}{2}$ " i.d. by 10"

used to remove the insulation from the inside of the wire. Several slow and unsuccessful methods were tried before it was found that coarse sandpaper placed on a flat, narrow piece of material with a long handle could be used to abrade the inside surface of the wire. This method quickly removed the insulation along the length of the slot. It is essential that good contact be made between the wire and the sliding contact, to prevent noise and detuning.

spaced 120 degrees apart. The ends of the wire are fastened under one of the screws at each end of the coil. The electrical circuit of the antenna is shown in Fig. 2.

## CONSTRUCTION AND ASSEMBLY SUMMARY

The coil is wound with 175 turns of No. 18 enameled wire. The winding just covers the slot. The inductance with the slider all the way to the top (approximately 2.8 Mc.) is 120 microhenrys, with a Q of 150. About 80  $\mu$ H. is used at 4 Mc. Before the coil is wound, the form is sprayed with Krylon to reduce the effects of moisture. Several coats are later sprayed on the completed coil to help hold the wire in place and for atmospheric protection.

The inside of the coil wires must be well cleaned. This will prevent detuning during transmissions and eliminate "intermittents" during reception. A good snug fit in the bearing plug will aid in maintaining good contact between the slider and wire.

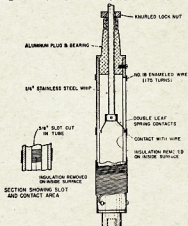


Fig. 1—Cutaway drawing showing the construction of the loading coil. The dimensions can be varied to suit materials available.

long. A longitudinal slot  $\frac{1}{8}$ " wide by  $\frac{1}{8}$ " long is cut in the tube. The ends of the slot are equidistant from the ends of the tube. Contact between the slider and the inside of the wire is made through this slot to provide tuning adjustment.

The slider contacts were made from heavy-duty spring contacts obtained from a defunct Centralab JV-9002 switch. Two of these are soldered 180 degrees apart to a collar which is then fastened to the main whip with set screws. One spring contact rides on the inside of the fibre tube and provides electrical and mechanical stability. The other contact rides on the inside surface of the wires, which have been cleaned of insulation.

Because of the danger of shorting turns, a chemical cleaner could not be

External view of the coil, whip bearing and locking system.

Additional support for the whip, to help prevent the contact on the wire from moving, is provided by a fairly long bearing at the top of the coil. The aluminium plug and bearing is about 2 $\frac{1}{2}$ " long. The hole to pass the whip rod is a snug fit to help hold the contact secure. A Millen No. 10062 shaft lock holds the whip firmly in position after tuning to the desired frequency. The loading coil is secured to the base section by another aluminium plug tapped for  $\frac{1}{8}$ -24 thread. Both of these end pieces are fastened to the inside of the fibre tube by three 8-32 machine screws

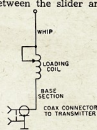


Fig. 2—Electrical circuit of the whip antenna with loading coil.

The whip is marked for the various bands and frequencies, which are then permanently stamped in the proper places. It was found that the 75 metre phone band could be covered with two settings, by tolerating a slight power loss at each side of a centre frequency. The other bands were calibrated at only one setting. This permitted optimum adjustment for any frequency within a given band. When operating on the 75 metre band the slider is set near the top, while on 10 metres the slider is at or near the bottom of the coil.

The antenna loading coil system shown in the photograph has been used for about six months under all conditions with good results. No detuning or noise has been experienced. Power as high as 60 watts into an Elmac AF-67 has been used without any difficulty.

This antenna tuning system has solved most of the problems encountered with tapped coils, outside sliding contacts, cumbersome LC tuners and others. It is small, neat, stable and, after calibration, easy to adjust to resonance on any band.

No measurements of any sort other than those mentioned above have been made on the coil. Successful QSOs are being made and it is felt that this provides a good indication of its operating characteristics.

\* Reprinted from "QST," April, 1962.



# High Altitude Nuclear Explosion at Johnson Island and Associated Effects on H.F. Signals at Hobart, Tasmania

LEN EDWARDS,\* VK7LE

WITH the news some months ago that the U.S.A. intended to explode a number of nuclear devices at various altitudes above Johnson Island in the Pacific Ocean for the purpose of observing effects on radio communications, it was considered probable that some disturbance to long distance h.f. communications would be observed in Hobart on signals whose path passed close to the area.

After considering the problems involved it was decided to make an attempt to observe any such effects and in order to get maximum information from the observations, the following basic requirements would be necessary:

- (1) As many frequencies as possible should be observed.
- (2) The transmission path should pass through or close to the explosion area.
- (3) The observed stations should transmit for the full 24 hours each day.
- (4) A time standard should be available for accurate timing of any observed effects.
- (5) Received carrier strength and modulation should be observed.

The equipment available for the observations was three receivers, one twin-pen recorder, and two magnetic tape recorders, thus limiting the number of observed frequencies to two, and after a search for suitably located stations, it was found that the WWVH transmitters run by the American National Bureau of Standards and located at the Hawaiian Islands admirably fulfilled all requirements.

WWVH transmits continuously on frequencies of 2.5 Mc., 5.0 Mc., 10 Mc., 15 Mc. and 20 Mc. The modulation consists of standard frequency tones and one-second standard timing pulses which are controlled within very fine limits and therefore eminently suitable for timing any observed effects.


The signals at Hobart from these stations were checked on the various transmission frequencies and it was found that 10 Mc. and 5.0 Mc. were the only frequencies consistently received, the 10 Mc. signal being received with good strength between 2 p.m. and 5 a.m., a total of fifteen hours each day, and the 5.0 Mc. signal was received for approx. twelve hours each day from 4 p.m. to 4 a.m. These frequencies are shared on an international basis by frequency standard stations in other parts of the world, and at certain times other stations were received along with WWVH, however as all have carrier frequencies controlled to international standards no heterodynes are evident.

The stations were constantly were JYJ in Tokyo, WVV in Washington, BPV in Peking and HBN in Switzerland.

land. Most of the time the signal from WWVH was predominant and readily identified on the chart by the carrier break of several minutes at 15 minutes past each hour.

This carrier break provided a ready time check on chart speed and also a check on the relative strength of other stations on the frequency during the off-air period. The audio output of each receiver, consisting of standard time signals, was fed to tape recorders which were switched on five minutes before the expected time of the explosion.

The rocket launching which finally resulted in the successful explosion was scheduled for 0900 hours U.T. on 9/7/62 (U.T. being essentially the same as GMT). Rocket lift off occurred at approx. 15 minutes before detonation of the device and the flight apparently continued normally until "zero" at 0900 hours. The start of the count-down zero time pulse coincided with the 0900 time pulse from WWVH, and although the count-down pulse appeared to be cut short and disappeared with a burst of static, the signal from WWVH

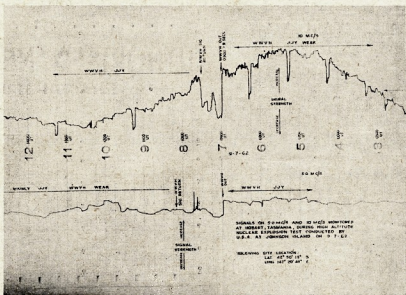

Pen recordings showing effects of high altitude nuclear explosion at Johnson Island on 10 Mc. and 5.0 Mc. signals received at Hobart from station WWVH in Hawaii. The sharp cut-off for both frequencies at the time of the explosion is clearly shown at 0900 U.T. (7 p.m. E.S.T.)

—Photograph by courtesy of VK7LJ.

Continuous charts of the signal strength on 5.0 Mc. and 10 Mc. were made for approx. six weeks before a successful launching occurred at Johnson Island, and during this time a daily pattern of signal strength was established for comparison with signals received during and after the event.

The third receiver was used to monitor the count-down which was broadcast on several frequencies by American stations in the area. These status broadcasts, operating under the code name "April Weather", gave details of the count-down on s.b. on frequencies of 4631 Kc., 9253 Kc., 12020 Kc., 15515 Kc. and 17473 Kc. It was found that 12020 Kc. and 15515 Kc. gave best signals at Hobart. It was noted that the count-down time signals appeared to be synchronised with the time signals radiated by WWVH.

on 10 Mc. continued until the 9th second pulse and then also cut out completely with a sharp click. Due to misoperation of the tape recorder the exact cut-off time of the 5.0 Mc. signal was not observed but the pen recorders on each frequency were observed to drop at the same time. Tape recorders showed that the signals from WWVH disappeared completely on both frequencies.

On 10 Mc. the signal returned weakly approx. 12 minutes later and then faded out again, gradual return to normal took place 32 minutes after the explosion, but faded again approx. 16 minutes later. It appears from the chart that WWVH signals were only present at 1115 UT and 1315 UT with little other evidence of signal for the rest of the night. The signal on 5.0 Mc. returned

(Continued on Page 19)

\* 10 Musgrove Road, Lindisfarne, Tasmania

## Further Modifications to the No. 122 Transceiver

I have read many reports of the lack of modulation, etc., in the ex-Service No. 122 Transceivers. The modifications I put forward are not mine, being group contributed.

When I first received my No. 122 set, I found the modulation to be both poor and noisy. After much searching through the modulator circuit, I found capacitor C4C to be at fault. This was replaced and the modulation and quality of same was considerably improved. I could now overmodulate the carrier. Another friend had similar trouble (low modulation and distortion) and by the replacement of this capacitor the set performance was much improved. C4C is in the plate circuit of V3A, a 1H6G, and is a by-pass to earth of 200 pF.

Another modification is to vary the size of the feedback capacitor C17A in the modulator circuit. The higher the value of this capacitor the less modulation gain, and vice-versa. In my set, with the feedback circuit cut out, the gain was too high, resulting in reports of microphonic modulator valves.

To get loudspeaker operation, solder a 0.01  $\mu$ F. 600v. paper capacitor, or similar, from the second lug from the chassis end on the side nearest the front panel of the driver transformer T4A. The other lead is then taken to the line jack, the lead is soldered to this jack after cutting the other lead off the line jack. A high impedance

speaker transformer is connected with a suitable speaker to the line jack. The output is quite satisfactory, even for mobile work.

I found the sidetone a bit too high in level, so I "borrowed" relay RL4 contacts 26 and 27 to switch in a 22K half-watt resistor on transmit. This cut the sidetone sufficiently so that no feedback was evident.

The next one is for those who are not thrilled with pulling the unit to pieces to change crystals. I obtained an ordinary two-pole four-position Oak switch and fitted it in place of the original oscillator control. I had to completely strip the switches and rebuild them, as a switch of sufficient shaft length is not normally available. I fitted the extra crystal socket on the front panel just above and to the side of the switch shaft. A word of warning here! Make sure there is very little capacity coupling between the two wires or your crystals may not oscillate.

Fitting a co-aerial aerial socket is a must and this can be fitted near the meter.

There are many modifications that can be done to these sets, many of which have been published in earlier editions of "Amateur Radio". (These include "Wireless Sets No. 22 and 122" July 1959; "Hint to 122 Transceiver Owners" April 1960; and "Modifications to No. 122 Set," January 1962."—Editor)

These sets are not the easiest to work on, but with care everything can be got at, and the resulting performance after modification makes it worthwhile.

—Rodney D. Champness, VK5ZCD.

## Fools' Modulation

NOT everyone agrees with this explanation of f.m. as some people think it is a fine mode to use.

F.m. is now being used on 2 metres by Melbourne Amateurs and interest is certainly increasing.

Equipment being used is mainly of commercial origin, but don't despair changed P.M.G. regulations will remove from commercial service a lot of gear ideal for Amateur use. However, a v.f.o. and reactance tube works nicely and the evergreen 522 is a natural for f.m. net use.

The f.m. network frequency in Victoria is 145.854 Mc. Crystal multiplication to achieve approx. 10 kc. deviation is 36. Audio limiting and a.g.c. are also used to maintain high average modulation levels. Receivers should contain two limiter stages as adequate limiting will provide best results. Remember there are less components in a limiter stage than an i.f. amplifier and an f.m. detector is not really complex.

F.m. is easily copied using slope detection with a conventional a.m. receiver, but don't condemn f.m. Under these conditions f.m. is only 25% as effective as an a.m. transmitter of the same power.

A good f.m. receiver should limit with a 1 microvolt signal giving a Readability 5 signal. With f.m., all signals are Readability 5 (unless there's little deviation) and signal strengths are weak or strong. Gone are the days of lament when you get S7 in return for your statement of \$9+ incoming.

Vertical polarisation is recommended which follows commercial practice of a quarter wave vertical whip antenna.

Mobile operation is most popular as interference (ignition, etc.) does not appear. This is most welcome. Most mobiles run 20 watts input to the 2E26 final and to the writer's present knowledge about 40 of these units are in Amateurs' possession. About 20 larger units (p.p. 2E26s) are known to be in Amateur hands and in the process of conversion, some running inputs as high as 120w.

This f.m. net (145.854 Mc.) will, I feel, expand rapidly and provide an excellent basis for W.I.C.E.N. or emergency use.

Is a.m. better than f.m., or is h.f. better than v.h.f.? No matter what your answer is, all modes and all bands should be used.

Care should be taken to ensure that all 2 metre f.m. stations operate on the correct frequency.

If any information or assistance be required, please contact the writer A. J. Stewart, VK3ZFS, 11 Woodstock Rd., Mt. Waverley, Vic. or J. Spicer, VK-3ZEL, 413 Stephensons Rd., Mt. Waverley, Vic.

Conversion of the 522 for f.m. use is planned and details will be published as soon as possible.

—VK3ZFS.

## BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY AND OUTPUT



Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:—

6280, 4095, 4535, 2760, 2524 Kc.

5.500 Kc. T.V. Sweep Generator Crystals, £3/12/6.

100 Kc. and 1000 Kc. Frequency Standard, £8/10/0 plus 12½% Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on Application.

455 Kc. Filter Crystals, vacuum mounted, £6/10/0 each plus 12½% Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 AND 7 Mc. BAND.

Commercial—0.02% £3/12/6, 0.01% £3/15/6, plus 12½% Sales Tax.

Amateur—from £3 each, plus 12½% Sales Tax.

Regrinds £1/10/-.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carrel, Box 2102, Auckland. Contractors to Federal and State Government Departments.

## BRIGHT STAR RADIO

46 Eastgate Street, Oakleigh, S.E.12, Vic.

Phone: 57-6387

With the co-operation of our overseas associates our crystal manufacturing methods are the latest.



# AN EFFECTIVE NOISE SILENCER\*

## USING A SEPARATE NOISE RECEIVER

G. T. SASSOON, G3JZK

IN the design of many of today's communications receivers, a much neglected feature is the noise limiter. This is possibly due to the fact that commercial users can pick their QTH, and therefore are not likely to be troubled by ignition noise to the same extent as Amateurs—a fact of which the designers of many specialised Amateur-band receivers do not seem to be aware. Furthermore, the increase in road traffic makes the ignition noise problem still more acute, particularly, of course, to the mobile worker.

The deficiencies of the conventional diode clipper-limiter type noise suppression circuit are well known. At best, they are barely effective on weak phone signals, and almost totally ineffective on s.s.b. Various solutions have been proposed: the Lamb noise silencer (first described in "QST" for Feb. 1936) is a lot more effective, although still suffering from certain inherent disadvantages; and, more recently, the Collins Radio Co. have marketed a silencer similar in principle to that described here. However, neither circuit seems to have achieved much popularity on this side of the Atlantic, so the present article may be of some assistance to fellow-sufferers from ignition QRM.

### PRINCIPLE OF OPERATION

Consider the block diagram of Fig. 1. A noise pulse radiated by a car's ignition system is picked up by the noise and main aerials simultaneously. It is amplified and detected by the noise receiver, which operates at about 40 Mc., and the rectified impulse is then used to trigger a monostable flip-flop circuit. This produces a long, negative-going pulse, which is applied to the balanced gate in the main receiver i.f. chain, so as to switch the receiver off for a period. In the meantime, the noise pulse has also been coming through the main receiver front-end. However, the bandwidth of the latter is comparatively narrow—a few kilocycles, as compared with over a megacycle for the noise receiving section. Therefore the noise impulse will take some time to build up to full amplitude at point D—much longer than it takes at point C. This is illustrated in Fig. 2. Thus, it is evident that the silencing impulse will have cut off the gated stage some time before the pulse arrives via the main receiver at point D, and so the net noise output from the gated stage at E will be very little. What we have done, in effect, is to switch the receiver off for the duration of the noise pulse.

This system works very well, but there are a number of critical points about the design which must be taken into consideration. First, every precaution must be taken to maintain the highest possible bandwidth in the noise

● This interesting article describes the practical application of noise quenching to an Amateur-band receiver, and is based on the sophisticated Collins design for QRN suppression, known as the Noise Blanker. An essential factor in the success of the unit described here is the R.C.A. 7360, a valve of an unusual type with special characteristics. Our contributor has been obtaining very satisfactory results with this noise suppressor for some two years, and has used it successfully on v.h.f. as well as on the h.f. bands. It is an important development in contemporary Amateur-band receiver design. — Editor, "The Short Wave Magazine."

receiver; this has necessitated the use of two pentodes for the flip-flop, where otherwise a double triode might have sufficed. Also, the first half-cycle of a noise pulse could be either positive-going or negative-going at the detector input; for this reason, it is necessary to use a full-wave detector.

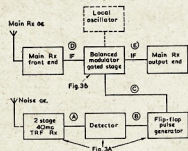


Fig. 1—Block diagram of silencer and associated receiver. The circuit arrangement is explained and discussed in the text. The local oscillator is included if the gated stage is also serving as a frequency-changer.

Secondly, if the bandwidth in the noise receiver is made high enough, then the silencing pulse itself will contain components at the i.f. Therefore, if a single-ended gated stage were used, the silencing pulses would appear in the output, defeating the entire purpose of the unit. If a low-pass filter (cutting off signals at the i.f.) were placed (say) at point C in Fig. 1, the bandwidth would be too small and the silencing pulses would arrive too late. For this reason, a balanced gate is essential; it must be set up so that no component of the silencing impulse can appear in the output. In practice, the balanced gate proved to be the most difficult part of the design and, in fact, a satisfactory solution was not achieved until the R.C.A. 7360 became available.

The primary objection to this silencer as regards fitting it to existing receivers, is that it is necessary to break into the i.f. chain. There is no real solution to this problem and, even if there were, it would be most difficult to prevent the stray coupling which would enable the noise pulses to bypass the gated stage. Ideally, the unit should be built in conjunction with an outboard i.f. strip. The balanced gate may also be used as a frequency-changer, simply by feeding in a local oscillator signal in parallel with the silencing pulses, and taking output at the desired frequency. It is hoped in due course to use the existing unit in this way to change from 450 kc. to an 85 kc. i.f. This can be done by feeding in a crystal-controlled signal at 535 kc. and installing an 85 kc. transformer on the output side.

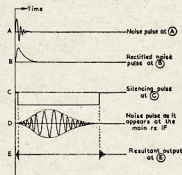


Fig. 2—Waveforms of a noise pulse as it appears at various points in the block diagram, Fig. 1.

In operation, the unit is most effective on s.s.b. signals, and when listening on those (rare) spots on the h.f. bands where there are no signals. On c.w. the holes are occasionally noticeable, particularly when they occur in the middle of a dash; however, only at the highest speeds could this cause a dash to sound like two dots. On strong a.m. signals, however, the holes are distinctly audible, particularly when it is necessary to increase the hole length to cope with the noisier vehicles. Nevertheless, the amplitude of pulses present in the output cannot exceed that of 100% modulation of the incoming carrier, so that the performance of the unit at its worst is equivalent to that of an ordinary diode clipper at its best. On weaker a.m. signals, the holes are much less noticeable, and under no conditions do they make copying difficult.

### CIRCUITRY

The noise receiver front-end (Fig. 3a) uses two 6AK5s, with conventional circuitry. Only two stages are necessary to give the required gain; owing to the broad-band nature of noise, the

\*"The Short Wave Magazine," August, 1962.



noise output is proportional to bandwidth as well as to gain. This receiver has a bandwidth of about 2 megacycles (about 200 times that of a normal receiver), so only about 1/200 of the gain is required. The noise aerial can be any odd length of wire, although a vertical dipole placed strategically low down and near the road gives best results. (A 40 Mc. dipole is about 10 feet long, to save you working it out!) It is advisable to break the aerial connection to the unit when transmitting, to avoid damaging the r.f. stages with excessive grid current.

The anode of V2 is inductively coupled to the full-wave detector D1, D2: gain is deliberately sacrificed here by using a step-down at L3, to improve bandwidth. A negative-going pulse is delivered to the grid of V3, which is normally conducting. As a result, the anode of V3 delivers a positive impulse to V4 grid, V4 being normally cut off. If this impulse is sufficiently large to make V4 conduct, a negative impulse appears at its screen, which is fed back via the detector circuit and C16 to V3 grid, and the state of affairs reverses itself; V4 conducting, and V3 being cut off.

After a time, determined by VR1 and its associated 100K resistor R8 and 200 pF. condenser C16, the circuit reverts to normal. This produces a negative-going pulse at the anode of V4, the length of which is controlled by VR1. At the same time, a positive pulse appears at V3 anode, which is used to light a neon lamp, NE1. (This helps to fill up the panel, and gives an indication of when the unit is working.)

The negative impulse from V4 anode is fed to the control grid of the 7360 (Fig. 3b), which also has a diode (D3) fitted to protect it from positive-going surges, as recommended by the makers. The i.f. input is fed to the deflector electrodes of the 7360, balanced circuitry being used, since it gives a slight improvement in performance. (If, for any reason, this was inconvenient, it could probably be dispensed with.)

Cross-neutralisation is employed between deflector electrodes and anodes, using Philips' trimmers, VC1 and VC2, mounted on stiff wires over the valveholder. This is not strictly necessary to prevent instability, but is included to counter signal feed-through when the valve is cut off. Similarly, it is necessary to take every possible precaution to keep input and output isolated from each other. The input and output i.f. transformer, IFT1 and IFT2 (Fig. 3b), should be placed some distance from the valve, and the anode and deflector connections made with twisted pairs of wires. Using this ex-

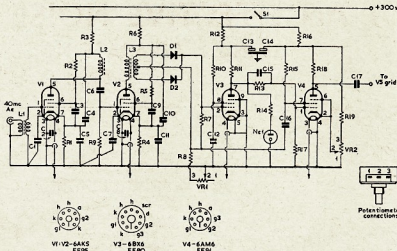


Fig. 3a—Circuit diagram of 40 Mc. noise receiver and pulse shaper, the output of which drives the gating unit—see Fig. 3b. In the arrangement shown here V1, V2 constitute the broad-band v.h.f. receiver, in which D1, D2 form a full-wave detector. As explained in the text, the action of the circuit is to produce a negative-going pulse at the anode of V4, the length of which is controlled by VR1. The neon NE1 is merely an indicator, and will absorb the positive pulses. The general inter-connection into the main receiver is shown in the block diagram of the system, at Fig. 1.

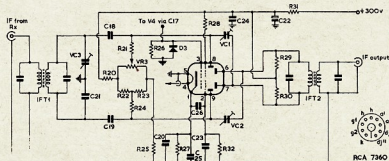


Fig. 3b—The balanced gate unit, incorporating the 7360, which is driven by V4 in Fig. 3a. VC1, VC2 are neutralising trimmers, and the adjustment and setting-up procedure are discussed in detail in the text. When the silencer is working properly, there should be an absolute blanking of peaky-noise signals, such as car ignition. G3/ZK has used the circuit for the last two years with great success, in a very noisy main-road location.

Table of Values for Figs. 3a and 3b.

C1, C2, C3, C1985, C19
---



pedient, it was found possible to do without full screening.

The i.f. transformer connections shown on the input and output sides are only suitable if the unit is to be connected by short lengths of coax. Otherwise, matching arrangements must be made, preferably including a cathode follower on the output side.

Chassis layout should be logical, with plenty of space left between stages. This is frequently as effective as sub-chassis screening for preventing instability. All power connections should be made with screened wire, and all r.f. stage heaters decoupled at the pins. Apart from the messy agglomeration of components round the 7360 base, the unit should present few problems constructionally.

## ALIGNMENT

After assembling and checking all wires, insert the 7360, connect up the i.f. leads, and switch on. If all is well, signals should be audible. Tune in a strong station and peak up the i.f. transformers with VC3 (Fig. 3b) at the middle of its travel. Then connect

oscillate provided that the layout is sensible, all decoupling condensers are present, and the coils are in cans or otherwise isolated.

When the noise receiver is functioning correctly, plug in V3 and V4. The neon, fully lit hitherto, should go out. If VR2 is advanced (clockwise), the neon will light brightly to the accompaniment of a high-pitched squealing from the loudspeaker. Bring VR2 back to a point well below that where the oscillation ceases. The unit should now work after a fashion, but it is still necessary to adjust the balancing controls at the 7360. For this purpose, a test signal is necessary. This is most conveniently provided by an unsuppressed vehicle parked as close as possible to the noise pick-up aerial and ticking over. (However, caution should be exercised in using this method if the vehicle is on the road, since it is an offence to leave it unattended with the engine running. So unless the XYZ can be persuaded to go and sit in it, something else must be found; possibly an electric buzzer or bell left running would suffice.)



The noise silencer unit as designed and constructed by G32K and fully described in the article. Once adjusted, and incorporated into the main receiver, its operation is automatic. It will give almost complete noise suppression and within certain limits the higher the stray noise level, the more effective the action of the limiter. It is based on an advanced and very sophisticated design used commercially by the Collins Radio Company.

a 223-volt dead-air battery between 7360 grid (negative terminal) and earth (positive terminal). This should cause an appreciable falling off in signal strength. Adjust VC1 and VC2 (the neutralising trimmers) for minimum signal. Disconnect the battery. The stage should now function again, amplifying strongly; it should give at least 70 db. reduction in signal when the battery is connected.

Next, the noise receiver should be aligned. Plug in the 6AK5s, and connect headphones across the 27K resistor R7 at V3 grid. Noise should be heard, increasing when the aerial is connected. Peak-up the cores of L1, L2 and L3. The exact frequency chosen for this is not critical; the most important consideration is that there should be no non-noise signals in the passband. (At Cambridge, a frequency just i.f. of t.v. Channel 1 Sound is quite satisfactory.) With good h.r. phones, ignition noise should be uncomfortably loud when the stages are correctly aligned. If no output is obtained, check for oscillation by connecting a voltmeter in place of the phones. However, the unit should not

Thus provided with a steady noise signal by one of these methods, the neon should flash regularly, and there should be a clicking from the receiver. To adjust the balance, back off the r.f. gain on the main receiver, and turn up the i.f. unit gain as much as possible. There will probably be a considerable amount of noise. Adjust VC3 and VR3 for minimum output; try touching up the neutralising trimmers if the null is not very sharp. Then return to normal listening conditions, peak up the i.f.s., and repeat the battery test to make sure. The unit should then be fully functional, producing virtually no noise when there is no input signal, and blocking any signals completely when cut off by the battery.

When finally it is working, the only indication you should ever receive of passing traffic will be a frantically flashing neon.

## ABOUT THE 7360

As a postscript, a few words about this valve might be in order, although the makers' agents—R.C.A. (Great Britain) Ltd., of Sunbury-on-Thames—will provide full information on char-

acteristics and suggested applications. They are somewhat expensive, 55/- (Sterling) each about two years ago, but worth it in that they permit considerable circuit simplifications. They consist in principle of an electron gun, a pair of deflecting electrodes much like those in a c.r.t., and a pair of anodes. The gun projects a sheet beam of electrons between the deflectors, on to the anodes. When the deflectors are at the same potential, each anode receives an approximately equal share of the current. Any difference in deflector potential causes the relative anode currents to change, whereas if both deflectors are changed in potential by the same amount, the anode currents are virtually unaffected. At the same time, the total anode current can be modulated by the control grid. This valve lends itself to numerous applications. For example, it could be used as an audio phase splitter, with earthed control grid, audio input to one deflector, and outputs from the anodes.

However, its principal application is for balanced modulator use in s.s.b. equipment; for this purpose it is of considerable value, since it makes it possible to build a balanced modulator with two single-ended inputs.

## ERRATUM

The author of "A 100 Watt P.E.P. Band-Switched Phasing S.S.B. Transmitter" (October 1962) has drawn attention to an error in the circuit on page 4. The 50 pF. coupling condenser in the output pi-coupler should be 500 pF.

## W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. New members and those whose totals have been amended will also be shown.

### PHONE

Call No.	Cer. No.	C't-ries	Call No.	Cer. No.	C't-ries
VK6RU	2	281	VK3WL	14	211
VK3AB	45	275	VK3ATN	26	204
VK3XK	43	270	VK3JH	12	192
VK3AHO	51	263	VK4RW	22	184
VK4FJ	21	244	VK3GB	30	183
VK9KW	4	211	VK3JZ	61	180

### C.W.

Call No.	Cer. No.	C't-ries	Call No.	Cer. No.	C't-ries
VK3KB	10	307	VK3RP	56	229
VK3CX	26	291	VK3JH	12	226
VK3QL	5	279	VK3BZ	6	222
VK4FJ	29	274	VK2AGH	71	220
VK3NC	19	266	VK4H	8	218
VK6RU	18	240	VK3RX	23	216

Amendments:	New Member:
VK3XB 75 265	VK3JE 77 100
VK3ARK 66 263	
VK4SD 32 193	

### OPEN

Call No.	Cer. No.	C't-ries	Call No.	Cer. No.	C't-ries
VK3ACX	6	300	VK3AHO	76	266
VK6RU	8	290	VK2AGH	83	265
VK4FJ	32	283	VK4HR	7	233
VK6MK	74	273	VK3BZ	4	231
VK3NC	77	269	VK3JA	44	229
VK3HG	3	267	VK3WL	45	225

Amendment:
VK3TL 85 150

# IT'S NEW! IT'S NEW!

# AMATEUR RADIO HANDBOOK

BY R.S.G.B.

Price 56/3 and 2/6 postage

*This book provides a first class course of instruction for the intending Amateur Operator and a gold mine of reference for those already experienced*

A MUST FOR ALL ENTHUSIASTS!

AVAILABLE NOW FROM:-

## McGILL'S AUTHORISED NEWSAGENCY

Established 1860.

183-185 ELIZABETH STREET, MELBOURNE, C.1, VIC.

"The Post Office is opposite"

Phones: 60-1475-6-7



### UNIVERSAL SOUND

*A Product of Italy*

Model 601 is a Dynamic Unidirectional (Cardioid) Microphone for studios, music and public address, strongly built and famous for quality.


Output: —54 db. (1 volt p/microbar).  
Response: 50-12,000 c.p.s. unidirectional.  
Impedance: 25,000 ohms, easily stepped down to 250 ohms.  
High or low impedance selection.  
Dimensions overall: 60 x 60 x 155 mm.  
(2-3/8" x 2-3/8" x 6-1/8").  
Low frequency change switch for use when speaking.

### DYNAMIC CARDIOID MICROPHONE Model 601

Free of amplitude, phase and harmonic distortions. High and low impedance. It offers an additional discrimination factor with a difference of 18 db. from front to back.

On-off switch on handle.  
Detachable connector.

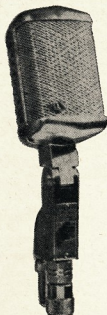Retail Price: £25/14/0  
Plus Sales Tax £2/9/0



Marketed by **ZEPHYR PRODUCTS PTY. LTD.**

**58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA**

**Phones: 25-1300, 25-4556**

# HETERODYNE FREQUENCY METER WITH CRYSTAL CALIBRATOR\*

## Design, Construction and Performance

E. PAWSON, VQ5IB/G8AP

**M**OST Amateurs at times feel the need of a reliable frequency meter and it is, in any case, obligatory to have a means of ensuring that the transmitter frequency stays within the Amateur bands. Although many modern receivers incorporate a crystal calibrator, there are considerable advantages in having a compact separate instrument, which includes both a crystal standard and a stable, calibrated wide-range heterodyne oscillator. Good quality frequency meters can be purchased—the BC221 is well known—but, even secondhand, they are not cheap. In any case, it is the writer's view that building such a piece of apparatus (and getting it working satisfactorily) is not only very interesting, but also very instructive.

Having purchased a Brookes 100 kc. standard bar, in vacuum mounting on a B7G base, and having obtained a 1,000 kc. crystal from a No. 48 Set, the author decided to build both these

into a crystal oscillator, and to put a v.f.o. (as a heterodyne oscillator) into the same box. While there is nothing new in this idea, nor in the circuits used, the detailed arrangement, and the results obtained, may be of interest to other Amateurs.

### FREQUENCY RANGE OF THE OSCILLATOR

Range switching was not considered acceptable, so attention was concentrated on a Clapp oscillator, of which the harmonics would be used on the higher frequency bands. This leaves one with the choice of covering most of the bands with rather poor bandspread, or providing mainly for the 7, 14 and 21 Mc. bands. The latter alternative was chosen, as good bandspread was considered essential; in addition, those three bands were of most interest at this station.

The heart of the instrument was to be the Edgystone 898 dial, the full traverse of which gives 500 scale divisions. It was finally decided to make

● This is a practical approach to a subject of interest to many an Amateur Radio operator—the provision of an independent, accurately calibrated and reliable frequency measuring unit. All such instruments—on our h.f. bands, at least—work on the principle of a variable frequency oscillator used as an external heterodyne wavemeter. The problem is to build and calibrate such an oscillator to the required degree of accuracy and stability. This article explains how it can be done on the Amateur work bench.

the calibrated range 3500-3600 kc. and to set the instrument so that this coincided with scale readings of 50 to 450 on the dial. Although the HO would, for convenience, be running on 3.5 Mc., its main function would be on the 2nd, 4th, 6th (and, to a lesser extent, 8th) harmonics. The following ranges would thus be spread over 400 scale divisions:


7,000	—	7,200 kc.
14,000	—	14,400 kc.
21,000	—	21,600 kc.
28,000	—	28,800 kc.

If it is desired to cover the 1.8, 3.5 and 28 Mc. bands adequately, the only real answer seems to be to capacity switching.
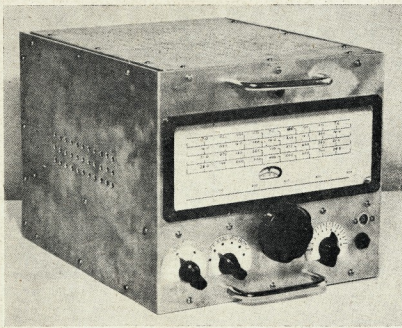
### CIRCUIT

One EF91 (6AM6), V2 in Fig. 1, is used in a conventional Clapp circuit, and a second EF91, V1, as a Colpitts crystal oscillator. A switch (S1) has been incorporated, so that either the 100 kc. or 1,000 kc. crystal may be switched in, together with their respective bridge condensers. In addition, a diode D has been put into the output circuit to improve harmonic content.

It will be noted that the capacity in the v.f.o. (h.o.) tuned circuit has altogether five components. C8 is the main tuning condenser of 13.5 pF. maximum capacity, while C9 in series with it reduces its capacity swing, and permits exact control of the degree of bandspread. C10 provides most of the padding capacity, and C11 allows a small fraction (about 3 pF.) of the latter to be controlled from the panel, for zero-setting the oscillator. Finally, C12 is the negative-temperature coefficient (n.t.c.) component, which materially improves the frequency stability. The inductance L1 is not adjustable.



The Heterodyne Frequency Meter as described in the article. It is capable of giving a high order of frequency measurement on the h.f. bands, provided the crystal calibrator can be accurately checked against WWVH. The crystal selector and function switches are on the left of the tuning control. The dial and tuning mechanism are of the latest Edgystone design, giving a wide sweep on the scale. Two crystal oscillator frequencies, of 100 and 1,000 Kc., are used and can be brought out separately; the zero-setting knob for bringing the instrument on to calibration is on the right.




At VQ5IB, a 320/6.3 volt power supply is on tap from an outlet on a supply receiver, so one 90 volt and one 150 volt regulator tube, V3 and V4 in series, were built into the unit. The crystal oscillator and v.f.o. thus draw regulated supplies at 240 and 150 volts respectively. The total h.t. drain is about 16-18 mA. The function switch S2 controls h.t. as follows: position 1, off; position 2, crystal on; position 3, v.f.o. on; position 4, both on.
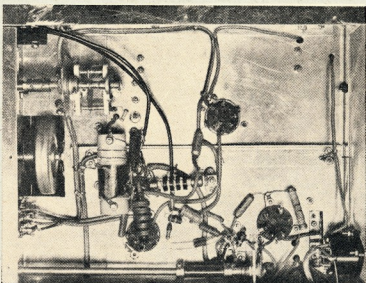
## CONSTRUCTION

The unit was built into a box  $9\frac{1}{2}$ " wide x  $8\frac{1}{2}$ " high, and  $1\frac{1}{2}$ " from front-to-back, constructed from 16 gauge aluminium—see photograph. The width chosen was about the minimum which would take the Eddystone dial. Doubtless each constructor will build the box in his own way, but it was found convenient here to bend one piece to form the front panel and two sides. The chassis (with only a narrow flange), back, top and bottom covers were then made from four separate pieces, fixed where necessary by means of angle strips. This made a good solid job, and the generous dimensions assist heat dissipation and enhance stability. To improve this further, a series of  $3/16$ " ventilating holes were drilled: 208 in the top cover, and 33 in each side above the chassis. A pleasing burnished appearance was achieved by giving the pieces a hard scouring with a power-driven wire brush before assembly.

Components and wiring are straightforward. The main dial is of best quality, and the tuning condenser C8 (13.5 pF.) is also a good quality Eddystone. The other expensive component



Under-chassis view of the Frequency Meter, showing general layout. The switch S2 (see circuit) is beside the dial-circuit flywheel, and the zero-setting condenser is above the coil. The power connections are carried in screened leads.

is, of course, the 100 kc. standard bar, but a first-grade crystal is essential. Apart from these, most of the items were home made or secondhand, in many cases obtained from surplus equipment. Except for C12, Philips concentric air trimmers were used for all padding and trimming functions, as a large number were at hand from stripped 88 Sets.

The crystal oscillator trimmers C2 and C4 (two Philips condensers each) are soldered through small silvered strips, which are then mounted on a perspex bridge over a slot in the chassis. C2 and C4 are thus isolated from each other and from chassis.

The zero-setting capacitor C11 needs to be only 2 or 3 pF. maximum capacity, so a little surgery was performed on an old 50 pF. variable. All except one pair of plates were filed off; these were bent a little farther apart, and the capacity was finally brought to a suitable value by soldering on, in series, a sub-miniature 4.7 pF. tubular ceramic.

The coil is wound with 26 gauge enamelled wire on a 1" diameter ceramic former, such as those found in 21 Sets. Some of these have wide-spaced spiral grooving: the tendency of the wire to slip into the groove was overcome by first covering the former with thin (0.01") polythene. Some experimenting was needed in the number of turns, but the size finally arrived at was 45 turns close wound, plus 3 turns spaced out over  $\frac{1}{2}$ ". The purpose of the 3 wide-spaced turns was to bring the wire to the end of the former, as this is made with the fixing holes at the extreme ends. After completing adjustments, the turns were anchored with polystyrene cement. The finished coil was mounted under the chassis on two short pillars, consisting of 4 BA bolts with nuts and locking washers.

The power supplies at 320 and 6.3 volts were brought into the back, through a recessed (safety) six-way socket, obtained complete with plug from a 38 Set. (These ex-Army units are extremely useful as a source of bits and pieces!) The output from the two oscillators is brought through low value fixed condensers to suitable connectors on the front panel, such as coaxial sockets or jacks.

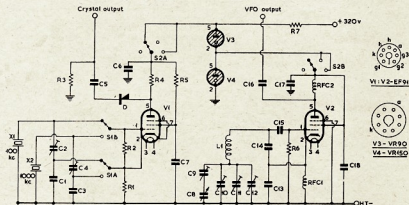


Fig. 1.—Circuit of the instrument described in the article. The circuitry associated with V2 forms the stabilised variable frequency oscillator, the coverage of which can be calibrated to a high degree of accuracy—see text. V1 is a c.c.o. with switched 100/1,000 Kc. crystals for marking and checking the variable oscillator; it can also be used as a separate 100/1,000 Kc. marker, giving band-edge and calibration beats into the receiver.

- C1, C13, — 0.001  $\mu$ F., silver mica.
- C14, — 220 pF. tubular ceramic.
- C10 — 60 pF. trimmer (two Philips concentric trimmers in parallel).
- C11 — 2 or 3 pF. variable (see text).
- C12 — 7.45 pF. trimmer, negative coefficient (N500).
- C15 — 100 pF. silver mica.
- C16 — 15 pF. silver mica.
- R1 — 16,000 ohms,  $\frac{1}{2}$  watt.
- R2, R3 — 0.5 megohm,  $\frac{1}{2}$  watt.

- R4 — 22,000 ohms,  $\frac{1}{2}$  watt.
- R5 — 100,000 ohms,  $\frac{1}{2}$  watt.
- R6 — 68,000 ohms,  $\frac{1}{2}$  watt.
- R7 — 5,000 ohms, 5 watts.
- S1 — Two-pole, two-way wafer type.
- S2 — Two-pole, four-way wafer type.
- RFC1 — 1.5 mH. r.f. choke.
- RFC2 — 2.5 mH. r.f. choke.
- L1 — 45 turns 26 gauge enam., close wound, plus 3 turns winding length  $\frac{1}{2}$  inch. Wound on 1 inch diam. ceramic former (see text).
- X1 — 100 Kc. standard crystal.
- X2 — 1,000 Kc. crystal.
- D — General-purpose diode, OA81.
- V1, V2 — EF91 (6A8E).
- V3 — VR90.
- V4 — VR150.



## SETTING UP

When using the crystal oscillator, e.g. when zero-setting the h.o. or calibrating, it has been found convenient to connect the crystal output socket to the receiver aerial socket. On the other hand, when using the oscillator as a frequency meter, it is often unnecessary to make any connection to its socket. It beats satisfactorily with incoming signals, or with the exciter unit of the transmitter.

After warming up the instrument for about half-an-hour, the station receiver was tuned to the 15 Mc. transmission of WWVH. With the crystal oscillator running at 100 Kc., trimmer C2 was adjusted to pull the frequency into zero-beat with WWVH during one of the unmodulated periods of transmission. The 1,000 Kc. crystal was then switched in and a similar procedure followed, using the trimmer C4. The two trimmers were then fixed with sealing compound.

The heterodyne oscillator was next adjusted for frequency and bandspread. With the help of the crystal oscillator, the receiver was first tuned to 7,000 Kc. The n.t.c. condenser C12 was set

zero-beat on 7,200 Kc. at a dial reading of 450. C9 was then fixed with sealing compound.

## TEMPERATURE COMPENSATION AND FINAL TRIMMING

The setting of the n.t.c. condenser C12 has to be done before the main trimmer C10 is finally set and sealed, because it forms part of the total padding capacity. The procedure adopted with the original model was as follows:

The n.t.c. trimmer having already been left at about quarter-capacity, the main dial was set at exactly 50, the functional switch at "both" and the power supply switched on. As soon as oscillation started (about 15 seconds), the zero-setter was used to bring the h.o. to zero-beat on 7,000 Kc., the time recorded and the instrument left running. At intervals, the main dial was altered to restore zero-beat, and the time and exact dial reading (estimated to 0.1 division) recorded. Suitable times were every five minutes during the first half hour, every 10 minutes in the second half hour, and thereafter every 15 minutes up to a total time of about 2½ hours.

When the drift test is satisfactory, the ceramic trimmer is left, the main dial set at 50, and the zero-setting control put at 60% of full scale. The main trimmer C10 is adjusted to give a zero-beat on 7,000 Kc. and may then be fixed with sealing compound.

## CALIBRATION

The v.f.o. is conveniently calibrated by running the receiver on the 28 Mc. band, and picking up each 100 Kc. harmonic of the crystal from 28,000 to 28,800 Kc. The heterodyne oscillator is first zero-beat on 28,000 Kc. with the tuning dial at exactly 50; at each of the subsequent 100 Kc. points, the zero-beat dial reading is accurately recorded. In addition, by tuning the receiver to the 21 Mc. band, four further calibration points may be picked up, corresponding to fundamental frequencies of 3516.6, 3533.3, 3566.6 and 3583.3 Kc. From the 13 points so obtained, a graph of frequency against dial reading is constructed. In order to do this, it is strongly recommended that a "flexible curve" be obtained to assist in the drawing. If this is used, and adequate care and patience exercised,

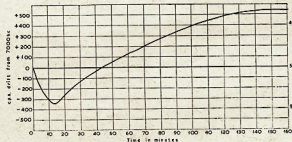


Fig. 2—The drift characteristic curve of the crystal-checked heterodyne frequency meter, in conditions as described in the text. As explained in the article, the shape of this curve can be varied according to the adjustment of the negative coefficient condenser. When a long warm-up run is possible, it is sufficient to check the scale against the crystal standard as readings are taken.

to about one-quarter capacity and left there during this series of adjustments. The series condenser C9 was set nearly at maximum, the main tuning dial at exactly 50, and the zero-setting control C11 at about 60% of full scale. The h.o. was then switched on and the padding condenser C10 adjusted to bring the frequency to that of the receiver. Then, with the h.o. and crystal oscillator both on, the zero-setting control was used to zero-beat the oscillator with the 7,000 Kc. crystal harmonic. (Note that it is necessary to bring the h.o. close to 7,000 Kc. before putting the crystal oscillator on, as otherwise zero-beats can be obtained with the oscillator tuned to the wrong 100 Kc. harmonic, even though the receiver is on 7,000 Kc.)

The main tuning dial was then set at exactly 450, and the receiver used to determine whether the oscillator frequency was above or below the 7,200 Kc. crystal harmonic. In accordance with the result, the series condenser C9 was slightly reduced or increased respectively. This whole process was repeated until the heterodyne oscillator was accurately zero-beat on 7,000 Kc. at a dial reading of 50, and accurately

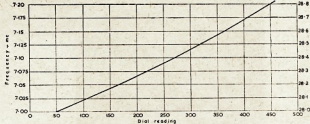


Fig. 3—The final calibration curve of the crystal-checked heterodyne frequency meter, as described in the article and shown in the photographs. From this basic curve, obtained from a specimen instrument constructed on the principles given in the text, graphs can be produced covering the higher frequency bands. Accuracy is limited only by the extent to which the crystal checker can itself be adjusted to zero-beat with some external frequency standard, such as WWVH.

The character of the drift can best be seen from a graph of the results, and one such example is reproduced here (Fig. 2). If the zero-beat reading goes appreciably above 51, or if it continues to rise after about the first 25 minutes, more n.t.c. capacity is probably required. On the other hand, if the zero-beat reading does not rise initially in the manner shown, or if the subsequent fall brings the reading much below 48, there is probably too much correction. The n.t.c. trimmer would then be adjusted in the appropriate direction and a new test carried out.

Readers not wishing to perform these experiments may obtain a simpler check. The instrument is switched on as before, the dial set at exactly 50, and the h.o. zero-beat on 7,000 Kc. It is then simply left running for two hours. At the end of this time, the dial is reset for zero-beat, and the reading noted. If this is above 50, the instrument requires more n.t.c. capacity; if it is less than 48, the n.t.c. capacity needs reducing. After making the necessary adjustments to C12, a new check is carried out. The instrument should, of course, be allowed to cool right down between tests.

a perfectly smooth and highly accurate curve can be drawn—see Fig. 3. For this purpose, the flexible curve is far better than sets of "french curves".

## DISCUSSION OF RESULTS

The 100 Kc. crystal was easily set to zero-beat with WWVH, and required about the expected amount of trimmer capacity (50 pF.). The 1,000 Kc. crystal obtained from the 48 Set, however, proved to be slightly inaccurate. After adjusting the trimmer as low as possible, it was still running 1.3 Kc. low on the 15,000 Kc. harmonic. The rotors were therefore removed altogether from the trimmers and this slight error accepted since, in any case, its main function is to provide 1,000 Kc. identification points.

Some initial trouble was experienced in getting the heterodyne oscillator to go off satisfactorily, and the cause was eventually traced to wrong constants in the tuned circuit. The dimensions of the coil had been worked out "according to the book," but L/C ratio actually present proved to be too high. After the coil had been pruned to the size given here, all was well.

(Continued on Page 18)

# A CLOSE-UP ON AWW

*The predominant brand line picture tubes sold in Australia are Super Radiotron. These tubes begin their life at the AWW factory at Rydalmere, N.S.W. Here, the following stages of production are closely supervised by a team of highly qualified engineers and technicians.*



## PICTURE TUBE MANUFACTURE



### Screen Preparation

Picture quality depends primarily on the excellence of the phosphor screen. In this air conditioned room the screen is deposited with the aid of super pure water and chemicals and the bulb is then prepared to receive its internal coating of aluminium.


*\*Detailed*

### Graphiting or Internal Conductive Coating

A general view of the conveyor system. On the right an operator prepares to internally coat certain areas of the bulb with special graphite mixtures, thus ensuring good connections between the outer button, the internal aluminium coating and the electron gun.



## AMALGAMATED WIRELESS


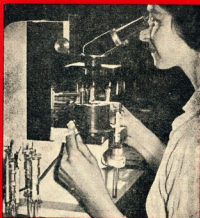


#### Alignment of Electron Gun

To produce an undistorted beam of electrons it is essential for the gids making up the gun to be concentric. Here an operator checks each gun for this requirement which ensures sharpest focus.
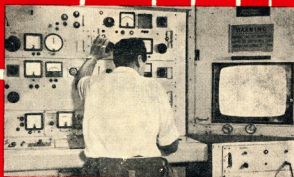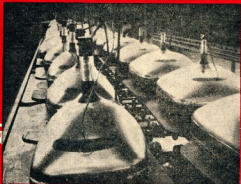
#### Aging

After prolonged heating in a near perfect vacuum the tube is stood off, bared and the electron gun run in or "aged" to give maximum performance and life when installed in a TV set.



#### Testing

All tubes from the production line are subjected to many operative tests at much higher voltages than they are ever likely to meet in the receiver operation. This margin of safety is built into all Super Rollotron tubes during manufacture.

**S VALVE CO. PTY. LTD.**  
**SYDNEY    MELBOURNE    BRISBANE    ADELAIDE**

Adjustment of the bandspread to exactly 400 scale divisions was quite straightforward and, when the setting was correct, the series capacity was estimated to be about 27 or 28 pF.

Calibration was also very satisfactory. The final calibration graph is reproduced here and does not suffer from cramping at any part of the scale; in fact, it is quite a pleasing approach to a linear relationship. For convenience in use, it is useful to enter on to the station calibration chart the 7, 14, 21 and 28 Mc. frequency scales. One minor, though interesting, feature is the slight reversal to a sigmoid shape which occurs near the top of the curve. At first, this was thought to be experimental error, but calibrations under other conditions gave the same indication. It was finally confirmed by an extra frequency observation at a dial reading of 500 (shown in the dotted portion of the graph). Calculations by the author have confirmed that this is not an effect caused by the presence of series and parallel capacitors, in association with the tuning condenser. The latter is nominally a straight-line-capacity type, but it is suggested that, as it nears its minimum, the approach of the unmeshed end of the moving vanes to the stator will slightly diminish the rate of decrease of capacity. This effect would be confined to settings near the minimum and would cause the peculiarity referred to. Over the calibrated range, there is no detri-

mental effect on the linearity of the curve.

The aspect which the author found most interesting was the effect of temperature on stability, and altogether 14 drift experiments were run. It is not necessary to give details of all these, but the main findings are summarized below.

The accompanying graph, Fig. 2, shows the drift characteristic in the final arrangement. The zero-beat dial reading, also the drift from the original 7,000 Kc. (dial maintained at 50), are shown plotted against time. During the first 40 minutes or so, the drift peaked to about -300 cycles and returned to zero. After that, it continued in a positive direction, reaching +500 cycles at about 130 minutes, when it flattened off and the frequency remained more or less constant.

When no n.t.c. capacity was used, the drift went continually more negative, and after only 30 minutes had reached -2.5 Kc. On the other hand, when larger amounts of n.t.c. capacity than that corresponding to the graph were introduced, the initial "valley" diminished or disappeared. The subsequent rise was then greater, reaching values of more than +1.5 Kc. The conditions illustrated by the graph therefore represent the best compromise, if one wishes to be able to use the meter soon after switching on. The graph shows that, for this degree of correction, if the meter is zero-beat

as soon as it starts to oscillate, and is also reset once to zero-beat after running about 80 minutes, it can be used the whole time after switching on, and will never be more than about 250 cycles in error (on 7,000 Kc.). That maximum error could be further reduced, of course, if one elected to carry out any extra zero-setting adjustments.

The above is the author's preferred approach but, if one wished, slightly less n.t.c. correction could be used, so that the eventual rise in frequency would be less. The initial "valley" would then be greater, and the instrument would only be usable after that stage had been passed. In the author's final arrangement, the n.t.c. trimmer had been adjusted to an estimated value of about 13 pF. (using type N500 trimmer).

To conclude the work, observations of temperature were made at two places inside the box: one close to the crystals, and one near the tuning condenser and ceramic trimmer. The temperature before use (and the room temperature) was 24°C. (75°F.). In five hours continuous running, the temperature only rose to 33°C. near the crystals, and 32°C. near the tuning condenser. No problems other than ordinary drift correction are posed by this nine-degree rise, and the 100 Kc. crystal would not change by more than 100 cycles at 7,000 Kc. (1½ cycles at the fundamental).

# BIG THINGS in SMALL TRANSFORMERS

Today the emphasis is on smaller components and our own lamination and heat-treatment section can cater for your special needs for small transformers. The illustration shows a typical example of a specially-developed low-level transformer in a Mu-metal case. Overall size is only 14" diameter by 11". This is one of the many special transformers designed and developed by our highly-skilled engineers.

ANOTHER

SPECIALTY

LM20

AT

# TRIMAX

## L M ERICSSON PTY. LTD.

TRIMAX DIVISION

FACTORY — CNR. WILLIAMS RD. & CHARLES STREET, NORTH COBURG, VIC. PHONE 35 1203.

Consult us for all small power or audio transformer requirements.



# SIDEBAND TOPICS—BUD POUNSETT,\* VK2AQJ

## MODIFICATION TO HIGH FREQUENCY FILTER

February "A.R." contained quite an amount of information on crystal filters and filter crystals. Arle Bles has sent along some further contributions to help you along the way to s.s.b. Arle refers to the high frequency crystal filter appearing in "Amateur Radio," Feb. 1963, page 9, Fig. 2. It has been found that the shape factor of the hybrid crystal filter can be improved considerably by the simple addition of a small trimmer across the input crystal F2 (see diagram, Fig. 1). The effect is a steepening of the high frequency side of the passband curve. Too much capacity will make that slope near vertical, but a new lobe higher in frequency will appear outside the normal passband. The proper setting therefore for this trimmer is only a few pF., say 5 to 10 pF. maximum, just enough to get the proper symmetrical passband without introducing a new filter lobe.

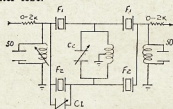


Fig. 1—Crystal Filter.

To tune the filter, tune for maximum output on  $\frac{1}{2}(F_1 + F_2)$ , set C1 at minimum required capacitance for symmetry in the band pass. Adjust C2 for flat top of the band pass.

## USING THE 5 Mc. FILTER

The transmitter block diagram (Fig. 2) and frequency table should be self-explanatory. A simple but very effective

\* 7 Thorpe Ave., Queanbeyan, 4S, N.S.W.

## S.S.B. CRYSTALS

Set of Five Gold-Plated  
Matched Crystals

Mounted in HC6U Holders  
Suitable for 455 Kc. I.F.'s.

Price £16-10-0 per Set  
+ 12½% Sales Tax

Full details on request.

BRIGHT STAR RADIO

46 Eastgate St., Oakleigh,  
S.E.12, Vic. Phone 57-6387

tive transmitter can be planned with a high frequency crystal filter. The use of overtone crystal oscillator frequencies higher than the operating bands will prevent a lot of trouble with spurious responses, birdies, unwanted mixing products, etc. With the frequencies as indicated, all three bands will tune the same way and only one v.f.o. range is required.

Those interested who have difficulties in procuring the required overtone

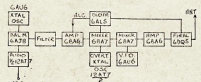


Fig. 2—Block Schematic of S.s.b. Transmitter.

Overtone Osc. Freq.	S.s.b. Signal	Intermed. S.s.b. Freq.	V.f.o. Range	Output Range
13850	+5500 U.S.B.	19350 U.S.B.	5350-5000	14000-14350 U.S.B.
17850	-5500 U.S.B.	12350 L.S.B.	5350-5200	7000-7150 L.S.B.
14350	-5500 U.S.B.	8850 L.S.B.	5350-5150	3500-3700 L.S.B.

Automatic sideband selection on each band, output frequencies tune the same way as v.f.o.

## High Altitude Nuclear Explosion at Johnson Is.

(Continued from Page 7)

weakly approx. 70 minutes after the event and remained very weak throughout the rest of the night.

It is therefore apparent that high altitude nuclear explosions do have an effect on long-distance h.f. circuits. This particular explosion occurred at an altitude of "hundreds of kilometres," probably in the ionosphere upper layers, and assuming the explosion took place on the count-down "zero," i.e. exactly at 0900, the signals from WWVH remained unaffected until nine seconds later. The fact that the signal path between Hawaii and Hobart passes several hundred miles south east of Johnson Island may help to account for this.

In the meantime, the next explosion is awaited with much interest so that further observations can be made. ●

## Phasing-Filter S.b. Generator

(Continued from Page 5)

In many phasing-type transmitters, even when the carrier-suppression controls are set to the optimum points, there is still a lot of residual signal.

crystals can write me direct, as for the crystals required for the filter and carrier oscillator.

## MECHANICAL FILTERS

Here is some interesting news in this field. We all know of the Collins product and that at least two Japanese firms are producing mechanical filters. One Japanese manufacturer even makes a filter especially for Amateur use at a very reasonable price, especially if you can buy it in Japan.

During a recent conversation with a UAI in Leningrad, I was told, to my surprise, that the mechanical filter in the UAI's transmitter was a product of the U.S.S.R. No more details were forthcoming but a little more may be learned at a later date.

Next month, I hope to bring you some interesting applications of Collins filters in transistorised equipment.

This is caused by the generation of low-frequency sidebands by the ripple frequencies of the high-voltage supply. Even when the last audio tube is removed, where parallel feed is used there still remains a circuit through which these low frequencies can circulate and so introduce sidebands at the ripple frequency in the output. Since the phasing system cannot suppress these low-frequency sidebands, it is essential to use maximum filtering in the power supply. A good double-section filter has been found necessary.

It is felt that the combination of phasing and filtering gives such good results with a minimum of pitfalls that it is well worth consideration by any home constructor. It is capable of results equal to those of any commercial unit, and the exciter will test the selectivity of any receiver. Best of all, the results are easy to duplicate as attested to by the fact that several successful conversions have been made.

Acknowledgments are due to KH6BCX who suggested the dual system so long ago that he will probably have forgotten about it; to VK2AJZ who constructed the "Package" on which all of the original experimental work was done; to VK2AST who complicated the subject by introducing mathematics; and to all others who can see any evidence of their work in this unit. ●

## P.A.C.C. CONTEST, 1963

V.E.R.O.N. (Vereniging Voor Experimenteel Radio Onderzoek in Nederland) invite Amateurs all over the world to take part in their seventh P.A.C.C. contest. The main purpose of their annual contest is to help Amateurs obtain the well known P.A.C.C. Award, for which QSLs or other written confirmation are needed of 100 different PA/PI stations.

Applicants for the P.A.C.C. Award will NOT have to submit PA/PI QSLs for QSOs made in the P.A.C.C. Contests, provided that their P.A.C.C. contest logs are in the possession of V.E.R.O.N.'s contest manager. If your PA/PI QSLs plus your P.A.C.C. Contest QSOs complete the 100 different worked PA/PI stations, you may send in your application, with QSLs, contest log details and three I.R.C.s to the V.E.R.O.N. Contest Bureau, P.O. Box 100, Amsterdam. The contest logs of the applicants will then be cross checked against the contest logs of the PA/PI participants.

There now are also stickers available for 200 and 300 different PA/PI stations worked. (P.A.C.C.-200 and P.A.C.C.-300)

### RULES

1. Contest Periods: C.W. April 27, 1963, from 1200 G.M.T. till 2.30. 26.3, 1800 G.M.T. till 5.0. Phone: May 4, 1963, from 1200 G.M.T. till May 8, 1963, 1800 G.M.T.

2. Frequencies: All bands between 1.8 and 30 Mc. may be used. Cross band contacts are not valid. (Attention: PA stations on topband are only licensed to operate between 1225 and 1235 kc.)

3. Procedure: Stations outside of the Netherlands will call "CQ PA", whereas PA/PI stations will call "CQ P.A.C.C.". Stations will exchange a six (five on phone) digit control number consisting of RST (RS) and the serial number of the QSO, starting with 001. PA/PI stations give after this control number two letters, indicating their province. The provinces are as follows:

GR, Groningen; GD, Gelderland; ZH, Zuid-Holland; FR, Friesland; UT, Utrecht; ZL, Zeeland; DR, Drenthe; NH, Noord-Holland; NB, Noord-Brabant; OV, Overijssel; LB, Limburg.

4. Points: Each QSO, confirmed by "R" or "OK", counts 3 points, 2 points are earned upon receiving the control number correctly and 1 point upon receiving the "R" on the transmitted control number. Unconfirmed QSOs may be completed by working the same station a second time. Each station may be worked once per band.

5. Multiplier: For stations outside of the Netherlands, the provinces give one point per multiplier for the multiplier, thus the maximum obtainable multiplier is 5.

6. Final Score: The final score is the sum of all QSO points from all bands, multiplied by the sum of all worked provinces/countries on all bands.

7. Entries: Multiband operation for stations outside of the Netherlands only.

8. Certificates will be awarded to the highest scoring stations in each country/district for c.w. and phone.

9. Contest Reports: The logs have to be filled in as follows: (1) Date and time (G.M.T.), (2) Stations worked, (3) Province worked, (4) Multiplier column for each band (fill in multiplier only if it is a new province), (5) Transmitted control number, (6) Received control number, (7) points.

Logs must be postmarked no later than 15th June, 1963, and have to be sent to Mr. P. v. d. Berg, PAOVB, Contest Manager V.E.R.O.N., Keizerstraat 54, Gouda, The Netherlands.

Each log has to be accompanied by a signed statement that the participant has observed the contest rules as well as the regulations for Amateur Radio in his/her country. In cases of dispute, the decision of the V.E.R.O.N. Contest Committee is final.



## Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the publishers.

### AWARDS FOR S.W.I.'s

Editor "A.B.," Dear Sir,

During 1961 I wrote to the VK Awards Manager seeking information re v.h.f. awards for S.W.I.'s and in reply, I quote, "I have to advise there is no certificate issued for S.W.I. reception by the Federal Executive."

At the same time I wrote to ZL land with the same request, and as I had the ingredients for a v.h.f. Award in that country, though, they may have one for S.W.I.'s. The reply was in the negative, but more hopeful than VK. I quote, "The matter of Awards for S.W.I.'s is receiving my attention and I hope to make an announcement by the end of the year."

Early in 1962 I again contacted the ZL Awards Manager and was told that the matter would be cleaned up by June or July of that year, and then it would be a pleasure to attend to my certificate requirements." I have just received a letter saying that my application for the 50 Mc. award will be accepted.

I feel sure that something in the way of an award similar to the "Elizabethan" or an S.W.I. equivalent of the W.A.V.K. could be arranged so as to create an interest for listeners.

New Zealand has made it possible, so why not give a thought for S.W.I. Awards in Australia?

—Chas. Abernathy, WIA-1211.

## DID IT WORK?

Mr. L. D. Rickaby, VK4VR, recently soldered together 65 empty beer cans in an attempt to produce a novel form of aerial. The cans were kept straight by placing them in a long wooden trough whilst solder, about a pound of it, was poured in the tops and bottoms.

The finished job was then mounted on insulators and is now adorning Mr. Rickaby's garden at Cooper's Plains, Brisbane.

The Beer Can Aerial is light enough to be held in one hand yet strong enough to stay up without guy wires. The aerial is equivalent to a piece of wire 33 ft. long.

Colin Grells (A3034), who told us about this aerial, has not yet been able to discover whether it has produced the DX results on 7 and 14 Mc. expected of it.

—Reprinted from the R.S.G.B. "Bulletin," December, 1962.

## Going to Auckland in June?

The New Zealand Association of Radio Transmitters is holding its National Conference in Auckland this year during week-end, 1st to 3rd June.

If any member of the W.I.A. anticipates being in Auckland during this period, they can make further enquiries from the Conference Secretary (Mark H. Churton, ZL1TB) as soon as possible at P.O. Box 9152, Auckland, N.Z. The registration fee is £N.Z.2/10/0 for the week-end's activities.

## VK3 RECEIVER FUND

The Victorian Division of the Wireless Institute of Australia wish to thank the following donors who helped to contribute towards the cost of the Collins receiver for use by VK3WI:—

R. A. Anderson, VK3WY.  
F. Ball, VK3XJ; J. Ball, VK3ABA; L. Banks, WIA-1096; J. Bell, VK3ABE; W. J. Bell, VK3WV; W. J. Bennett, VK3EJ; P. K. Bennie, VK3ZDP; R. A. Blake, VK3ZFM; B. Bosse, VK3AE; A. Bolton, J. Assoc.; A. E. Budge, VK3BB.

S. Clark, VK3ASC; H. CHF, VK3HC; A. D. Cook, VK3AUC; H. B. Dobbyn, VK3MF; J. Duncan, VK3VZ.

S. East, VK3ZLR; A. Elliott, VK3AEL.  
W. J. Falconer, VK3AWF; J. Fullagar, VK3AVY.

L. Guest, VK3GG.  
L. Harding, VK3AHL; F. W. Hebard, VK3HK; W. R. Kempster, VK3JY; J. Herd, VK3JK; W. J. Hewitt, VK3PH; A. Holst, VK3OH; M. Howden, VK3BQ; G. M. Hull, VK3ZS.

D. H. Jenkin, WIA-1309; R. Jepson, VK3AJ; J. Johnson, WIA-1599; A. Johnson, VK3ZMK; J. B. Kelleher, VK3AIK; J. I. Kelleher, VK3AIJ; J. P. Kelly, VK3AFD.

P. S. Lang, VK3ADN; I. Letic, VK3AIL; O. Lucas, VK3AVX.

A. V. Macey, VK3AZA; A. Mackiewicz, WIA-1313; H. C. Major, WIA-1312; G. Mallows, VK3AWM; C. Manifold, VK3EM; J. Matchett, VK3TL; A. H. Miller, VK3AH; B. Morris, VK3APM; G. C. Morrison, VK3TH; I. C. McKellar, VK3ZAL; J. McKellar, VK3AZM; D. McLellan, J. Assoc.; N. McLeod, VK3NM; C. McQuillan, VK3ACD.

P. Nugent, VK3AFN.  
P. O'Donnell, VK3ZU; M. Osborne, VK3ZCZ; M. Owen, VK3ZBO.

D. Paine, VK3PH; R. T. Pettigrew, VK3DO; K. E. Pinch, VK3AFJ; R. E. Pope, VK3ARP; W. M. Rice, VK3APF; K. V. Roget, VK3YQ.

W. G. Sargent, VK3SC; T. Savers, VK3AOG; P. S. Squire, VK3XK; I. Stoddart, VK3ZD; D. Stafford, VK3KS; H. N. Stevens, VK3JO; H. E. Stevens, VK3OJ; J. Symons, VK3JT.

R. Tandy, VK3KEJ; J. Tibbcock, WIA-1314; E. Tibbcock, WIA-1304; the late W. Tregear, VK3TX; J. Tutton, VK3ZC.

L. Utter, VK3AHU.  
P. Valler, VK3PF; G. S. Vincent, VK3AGV.

D. Wardlaw, VK3ADW; S. E. Widgry, VK3SE; S. J. Wilcox, VK3KC; H. G. Williamson, VK3CW; J. M. Wilbers, VK3ZO; R. Wooley, VK3JC; A. S. Woolnough, VK3BW.

W. Zimmer, VK3AWZ.

## DURALUMIN, ALUMINIUM, BRASS TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS 1" TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,  
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)  
Telegrams: "Metals," Melb.



HANSON ROAD,  
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)  
Telegrams: "Metals," Adels.

## FOR BEGINNERS:

# HEARING THE GOOD ONES

ALAN SHAWSMITH,\* VK4SS

WITH present patchy conditions on all frequencies, it is necessary to have all-band operation so that one can be listening on the best band at the right time. During the next two or three years, 80, 40 and 20 metres will be the best DX bands. Few if any can erect beams on 7 or 3.5 Mc., so it means we have to extract the most from single or phased wires.

### THE ANTENNA

To do this, we must firstly take a look at our allotment and consider its aspects. It is generally believed that the more wire out in space, results in greater r.f. pick-up efficiency. (This definitely proved to be the case in my particular location. Increasing the antenna length from 136 feet to 264 feet brought the weak signals, both on 3.5 and 7 Mc., right out of the hash.)

There is only one way to erect 264 feet in the average allotment, that is to have some of the long wire vertical and some horizontal. This is an advantage; if the antenna is to be used for transmitting as well, then the vertical section provides optimum angle of radiation.

The immediate question to ask about this is, does not such a length pick up QRN, etc. (Here again I can only answer for my particular location.) The answer is, no, when the wire is centred and resonated by an antenna tuning unit. This latter is a must, if one is to extract the most from a long wire. However, there is no place for dogma here, as each must find the antenna that best suits his needs and location. Generally speaking, then, it is best to get as much wire up, in clear space, as your allotment allows. In this way, too, directional effects are minimised.

One comparison can be made, for instance. For transmitting, a 7 Mc. ground plane antenna would be just as good as 260 feet long wire. Well up, but this latter will hear the weak ones when there is only QRN on the g.p.

### FIRST R.F. STAGE

So much for the antenna. The next important link in hearing the weak ones is the first r.f. stage of the receiver. It is here that the proportion of noise to signal is established. Each type of r.f. tube must be treated individually on its merits to see that it is doing its best. Many run this stage with 300/120v. plate and screen, and bias a little low, in order to get out the most.

### PROPAGATION

Before we go on to the optimum listening times, it is well to get the propagation picture clear for the various bands. Old Man Sol is sleepy at the moment. Sunspot activity is low, so a rough forecast for the bands during 1963 would be like this:

28 Mc.: A wash-out, generally speaking. During the pre-winter months

● Last year the author (Sub-Editor of the DX page) received more than one letter complaining that very little of the choicest DX could be heard. Why is it that some can pick up the best prefixes each month while others cannot? The latter usually blame their location, antenna or receiver, but this in fact is really only about half the reason, as many with only mediocre sky-hooks and receivers make out fairly well.

there may be openings to the tropic areas, mostly Pacific, brought about by E layer influence. However, during the winter, this, and to a lesser degree 21 Mc., will be devoid of DX signals.

21 Mc.: This band has prospects during the daylight hours. Pre-winter, there should be openings to the north and east, any time after dawn, but little after dark.

14 Mc.: This band has always been the DX man's "cup of tea". It is a 24 hour band, often, and long haul DX can be had at various hours. However, during winter the band becomes almost dormant at night and reverses itself during mid-summer, when it is best around midnight and worst at midday.

1.8, 3.5 and 7 Mc.: These are night bands. Once the sun is up, the DX disappears, both summer and winter. While the smooth sunspot number is so low, these bands are expected to improve, as far as DX is concerned. So for the next few years, if 14 Mc. falls off in activity, 7 Mc. might prove to be the best band for DX.

### OPTIMUM LISTENING TIMES

Half the best DX is missed by listening at the wrong times. Conditions cause band openings to vary, so no definite time pattern can be given, but the following may help.

21 Mc.: The pre-winter sequence of signals on this band in the past has been something like this. From dawn onwards the band intermittently opens to the East and Central America areas are prominent. Sometimes also the N/S circuit is operable and J and UA are loud and clear.

Shortly after midday this band has a habit of opening briefly to South Africa and South America, say around 0300-0430z.

During the afternoon Ws are often audible and when conditions are suitable (M.U.F. OK) around dusk signals from anywhere can appear. Europeans sneak through around 0800z.

14 Mc.: In the past this band has been so good at various times during the day and night, there are signals from all continents coming in at the one time. However, dawn usually brings an opening to the North West with Europe at good strength and sometimes L.P. to North, Central and South

America. Signals from this last named often travel 18,000 miles up and over via Europe and in darkness most of the way. This is from 1930 to 2200z.

Barring the winter months, 20 mx is usually poor during late morning and early afternoon. But often around 0330z and a little later (just as 21 Mc. does) the band opens to Central and South America. These signals are followed by a L.P. opening to Europe (via the South Pole). This circuit is much affected by solar storms, but nevertheless is fairly consistent when taken over a time period of one year (from 0430z to after dark E.A.S.T.).

The N/S circuit on 14 Mc. is often open day and night, but is usually much better during sunless hours. The N/S path lets signals through from J, and UA, but as the night progresses the path swings further to the West until Europe is audible on the short path. The band usually then reaches its peak some time after midnight (around 1500z), when various good prefixes can be heard from all continents except South America. (This latter is often good around 1030z.) The band suffers from a pre-dawn lull around 1800z when it is almost dead or the signals on it are hard to work.

3.5 and 7 Mc. are bands with very similar patterns to each other. 40 mx is the first to open to the East when Ws crowd in from 0730z approximately. 80 mx opens in the same direction a little later (0830z). After this, the N/S circuit opens up and J, UA, etc. show up, and are heard on and off through most of the night on 7 Mc. mainly. From 1600z, on both bands, the Europeans begin to show up, although they are hard to work on 80 mx. They are easier on both bands around 1930z. Sometimes the 7 Mc. band opens to Africa from 1700z on to dawn and also a L.P. circuit to North America appears around 2000z quite frequently.

For those who want some "snatch" times to hear DX, I suggest they "case" the bands just after dawn or just before dark. 80 mx through to 15 mx are prone to suddenly becoming good at these hours. Also, the time of 1030z (give or take an hour) is excellent. Signals appear from the Americas from VO2 in the north to VP8 in the south. That is almost from Pole to Pole.

All times given are GMT.

### APPROACH TO LISTENING

An attitude of impatience or haste is a sure way to miss DX—and unless one tunes very slowly, it is easy to pass over a weak signal that momentarily had dropped into the hash. It is better to listen for a while on a segment of the band rather than swing the dial over the lot. On 7 Mc. particularly, many good c.w. prefixes hug the first few kilocycles of the band.

DX is not the \$9 business it used to be. Conditions are such that the average signal is much weaker and has to be dug out, so tune slowly. ●

\* 35 Whynot Street, West End, Brisbane, Qld.



# A COMPLETE RANGE

for  
AMATEUR  
and

PROFESSIONAL  
COMMUNICATIONS  
FIELDS...

For World Wide Reception



**EDDYSTONE 840C:** A.C./D.C. Communications Receiver, frequency range, 480 Kc. to 30 Mc. Price: £111/12/7 (plus S.T.)

★ Send for technical brochure.

## "VICEROY" SSB EQUIPMENT for the AMATEUR



**KW VICEROY MKII TRANSMITTER**



**KW VICEROY MKIII TRANSMITTER**



**KW500 LINEAR AMPLIFIER**



**KW77 COMMUNICATION RECEIVER**

Complete station equipment as follows:

Viceroy MK II.—£204/15/0  
Power Supply for above £58/10/0  
KW500 Linear (p.s. inc.) £170/15/6  
Viceroy Mk. III. (p.s. inc.) £276  
KW77 Receiver £235

Nett, F.O.B. Melbourne, sales tax not included.  
Send now for full technical specifications.

**R.H. Cunningham**  
PTY. LTD.

8 BROMHAM PLACE, RICHMOND, VIC.  
and at Sydney, Brisbane, Adelaide  
and Perth

# LOW DRIFT CRYSTALS

FOR  
AMATEUR  
BANDS

ACCURACY 0.02% OF  
STATED FREQUENCY

3.5 and 7 Mc.  
Unmounted, £2/10/0  
Mounted, £3/0/0

12.5 and 14 Mc.  
Fundamental Crystals,  
"Low Drift,"  
Mounted only, £5.

THESE PRICES DO NOT  
INCLUDE SALES TAX.

Spot Frequency Crystals  
Prices on Application.

Regrinds ..... £1/10/0

## MAXWELL HOWDEN

15 CLAREMONT CRES.,  
CANTERBURY, E.7,  
VICTORIA

CHOOSE THE BEST—IT COSTS NO MORE



G. T. LEMPRIERE & CO. LIMITED. Head Office: 27-41 Bowden Street, Alexandria, N.S.W.  
and at Melbourne • Brisbane • Adelaide • Perth

# THE NEW "A.R." LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages  
with more writing space.

Price 5/6 each  
plus Postage

Obtainable from your Divisional  
Secretary, or W.I.A., P.O. Box 38,  
East Melbourne, C.2, Victoria.





Greetings fellow short wave listeners. With the advent of the winter months approaching us the daylight conditions should improve, at least we hope so. What this means now is the time to get that rx or antenna in working order. We complain of poor conditions at times, but how often have you tuned across the band and found perhaps one or two very DX signal on almost a dead band. Which goes to show that the band is at least active in some part of the world. How often have you listened during a Contest and heard the band full of signals? 28 Mc. for instance may not be as dead as most people think. On one occasion your scribe tuned across the 28 Mc. band and heard a South American station at 59 calling CQ, but nothing else was to be heard on the band. I know we are going through a poor period in regard to propagation conditions, but just because you can't hear much, don't always blame the ionosphere.

#### NEW SOUTH WALES

Don L2022 recently paid a flying visit to Melbourne. At present he is doing a spot of shift work on the local telephone exchange in Albany. Hope you get that QSL from Danny before long Don.

Chas. L2211 has again been hard at it. Just recently he received for the second time in two years, the Elizabethan Award for 50 Mc. Nice work, Chas. In the Ross Hull Contest, Chas. managed a very good score. However, a young friend of his has reported a bigger score that may take out the section. Chas. was last reported in the dial code in the Eddystone 640 and at the moment is busy shielding his 50 Mc. converter.

Chas. reports that at last the ZL boys have now made available a new award to S.W.I. This award is for confirmation of all ZL call areas on 50 Mc. Actually this award is the same as the man who has been awarded it was at the time of going to press, made available to Chas., but other claimants will have to wait until the award has been officially sanctioned, but unless you can show your grats to Chas on being number one claimant, and fine work on your behalf.

Now that the ZL boys have made this award available to S.W.I.s, we would very much like to see the W.I.A. to make the VK award available to S.W.I.s. There are no doubt some S.W.I.s who have heard all States on 50 Mc. (Any claimants?—Ed.)

Recently Chas received his certificate for the 1962 R.D. Contest. Nice going old son.

#### VICTORIA

You will all be interested to learn that the VK33 group has been asked to meet at 47 that was formerly used for VK3V1. We would like to thank Council for making it available to the Group. There still remains some work to be done on it, but this will be undertaken by the construction group, under the guidance of Ian Woodman. When the rx is repaired we intend to use it mainly for giving the newcomers an introduction to Amateur Radio. We will also give some of our younger members some idea on how to prepare a report for sending to the Y.R.C.

The construction nights are still proving popular under the expert guidance of Ian Woodman. It is only the young newcomers who are interested in the construction side of things, how about coming along to our evenings which are held on the second Friday of each month at 47B Victoria Parade, East Melbourne.

Attention all short wave listeners! The 1963 Short Wave Contest is under way. It starts after you read these notes. The date is the week-end of 6th and 7th April. The venue is Ballarat. On the Sunday we will be going through the studios. Also over the week-end we will be visiting a v.h.f. Ham shack as well as a h.f. shack. All in all, a most enjoyable and useful time. You have a chance to meet your fellow S.W.I. that you have heard about. An open invitation is extended to all S.W.I.s and any newcomers who might be interested. See you at Ballarat.

Newcomer to the S.W.I. ranks is Greg. Earl. Greg. has not been issued with an L number yet, but he is really doing well. He has got his rx and is very pleased with the results that he has obtained with it. His DX log is very good for a newcomer. Greg is using a 2000 dipoles with a switching system, and is very

pleased with the results he has obtained with it so far. When you have become more used to the HE30, Greg, we hope that you will soon have your name on the DX ladder with us. Hope you can get along to some of our meetings Greg., and make yourself known to the boys.

Craig L3093, who is our publicity officer, has been doing an excellent job giving S.W.I. notes over VKIWI each week. But it is up to us all to provide him with some information of our activities, so bear this in mind and drop Craig a line. His address is 10 Foch St., Ormond, phone number is LW 1773. Any news that you can forward will be very much appreciated.

Several years ago, we here in VK3 used to run monthly meetings. Due to lack of support we were forced to abandon them. We would like very much to re-introduce some activity along these lines. However it would keep complete waste of time to start again unless more interest is shown by members. So let us have your ideas on the subject. Remember the S.W.I. Group can only function successfully by each and everyone of us showing a keen interest toward the Group. If you have a gripe, don't be content to sit back and have nothing to say. We want to hear from you, the member, so don't be frightened to get up and have your say.

At present we have a monitoring watch on the 7 Mc. band. And if this proves popular it will be most encouraging.

#### QUEENSLAND

We are pleased to hear that our good friend Affon is at last on the improve after sickness and business troubles. Affon reports that conditions in Melbourne are now a lot better than poor now for some time. The only QSLs that he has received for many months have taken his total up to 82 confirmed. He is bemoaning the fact that he has not yet received a QSL which includes an I.R.C. and a S.A.E. He is getting very few returns. Yes we all are in the same boat, but unless you can show your grats to like to change it for a rx in the Rolls Royce class, one of these days. Best of luck to you old son, and hope that your dreams come

true. Thanks for the good wishes which are heartily reciprocated from this QTH. Very pleased indeed to hear from you again Affon and give my regards to all the boys.

#### SOUTH AUSTRALIA

Darrell L5041 has just joined our DX ladder. Very pleased to have you with us Darrell. During the Xmas holidays Darrell was in VK3 and reports hearing all VK call districts except VK6 on 7 Mc. using his transistor portable and a three-foot whip. He also managed to find time to get a few points in the N.F.D. Contest recently, and it is very nice to see a new name on the DX ladder. How about some of your other VK3 boys sending in some news of your activities?

#### WESTERN AUSTRALIA

Peter L6021 comes forth with another very interesting letter telling of his activities. Peter is using a Pye 8-tube rx as his hearing aid. He has been in the line-up for Phillips 6-tube rx. On 7 Mc. he is using a folded dipole, and on 14 Mc. uses one leg of the dipole. Judging from your reports Peter you are hearing plenty of it. Drew L6024 has been away for 12 cards for the month. Thanks for your very nice letter and look forward to hearing from you again next month.

Afton L2136/VK4 has these: VP4, KP4 and ZET.

73, Mac Hilliard.

#### DX LADDER

Countries	Zns.	S.s.b.	W
Conf. Hrd. Conf. Conf. Hrd. Conf. Hrd.			
E. Trebilcock	277	285	40
D. Granley	115	128	16
A. Westcott	85	159	31
M. Hilliard	71	217	33
M. Cox	64	222	29
J. Drew	48	184	24
C. Abernethy	47	95	28
N. Harrison	44	94	27
I. T. T. T.	42	184	24
P. Fields	26	133	—
D. Coggin	9	85	6
H. Burger	6	185	5

## YOUTH RADIO CLUBS

Good news from VK7 this month! Ian TZZ, Secretary of the VK7 Division, reports definite progress in Youth Radio Clubs at that State. Which has been appealing around—on that Division and is busy seeking co-operation and help in all directions, especially head-masters and teachers. Anybody who can keep their frequencies should help you, Ted.

Reg TZAO is a teacher at New Norfolk High and has begun the formation of a club there. Fern, TCV, is a teacher at Hobart Tech. High and giving the idea some thought. Some definite help from other locals would bring it about. The headmaster of Hutchings Grammar School has agreed to provide a room for a club, and ex-TSC, a teacher at the Friends' School (Hobart) is investigating the possibility there. The 13th Hobart Scout Group is working on the way and has a call sign, Father Burns, of Burnie Marist College, has a club under way. This college caters for boarders and such a club is sure to be desirable addition to the spare-time activities of the boys. Father Burns is contemplating the A.O.C.P., but would certainly appreciate some help from Burnie Amateurs.

Congratulations to all in VK7 who are directly helping. I hope all other VK7s will do the right thing and pull out those boxes of parts which have been sitting around for years. I can assure you that it is most important to make the early stages easy. Once the boys feel the fun and excitement of it, they won't be going to cost a fortune, the rest is easier.

A number of lads from St. Leo's College, Wahroonga, attended the Gosford Radio Club's Field Day on Feb. 17. Amostart was Harvey who has been at it for the A.O.C.P. and expects. Also at the Field Day was Ian Forrest (VK3AJF) the first A.O.C.P. from the Youth Radio Club. Fred (VK3JF) of Howards' excellent work at Booragui High. Keith

reports that seven ex-members of his club have moved into electrical and electronics vocations.

At VK1LS (Lynneham High) my own activity has been severely curtailed in the last year for health reasons, but the club stalwarts, George IGB, Roger Davis (hoping to get the A.O.C.P. in the few months), Ian Staines, Bill Tweedie, and Carl Brinkley (son of Tony ISG) do more than I do—a very healthy state of affairs. Roger has been sent away by his plate moulder an AT5 and make it behave itself. George is now in his final year of High School and has sent away to attend Amateur Radio time to concentrate on study. His goal is a maximum pass and Commonwealth Scholarship leading to B.Sc. As an incentive, gave him colour illustrations of the latest Collins gear—these are pinned up over his study desk! During the holidays, George has constructed a s.b. transmitter by the time you read this, it should be on the air—but at VK1LS! He is donating it to the club station until Nov. so that he won't be forced to leave his home. What will power! Anyway, we hope we're the first Youth Radio Station with s.b.s. entirely constructed by one of its members.

News is hard to get from VK3's 4, 5 and 6. Could it be there is none? Surely they can find a co-ordinator—despite the fact that this is a full-time job. Two very prominent VK3s told me in January that all the Y.R.C. information was neatly "pigeon-holed" and had no one in the Division, however, although a few brave souls had formed clubs.

And here's a challenge for VK3Pans—y'all take notice of talking of "band-wagons" and quoting the isolated enthusiast (whom we salute for bravery), why not find a Y.R.C. co-ordinator for the Division. We haven't heard of one yet.

Provocative 73, de Ken VK1KM.

## VICTORIA

50 Mc.: Ken 3ZLL is now active on this band. Ken is running 12 watts to a 6146 on approx. 50.75 Mc. and using a QQQ03 as a modulator. Stan 3ZDJ is now active and is re-appearing on the band, but this time will be using s.s.b. Glen 3ZBJ is active again and will leave from VK4. When he returns to the Sunshine State he will be located near the VK8 border and possibly will operate from that spot a number of times during the first week in December.

Activity, which was very low on 8 mX at the beginning of Feb., is steadily increasing. The Feb. 6 mX scramble was held on Sunday 24th. Unfortunately the control station did not put in an appearance, but the contest finally started with David 3QV acting as control. Only 4 stations completed, including two from the Geelong area. 3QV, 3ASG, 3ZAA and 3ZGM tied for first place in the city section with 8 points each, while 3ZMH won the country section with 9 points. The April scramble will be held on Sunday 28th commencing at 7.45 p.m. Join in.

144 Mc.: Bill 3ZLW has a new rig operating using a QQQ08/40 in the final. At first Bill had modulation troubles, but these have now been overcome. Rex 3ZVL, who normally provides a DX signal from Numurkah, has been holidaying in Melbourne and rag chewing most nights with the local gang. Bob 3ZRD has been QRMing during the last few days. His input and has replaced his "big wheel" antenna with an 8 element yagi.

The March 2 mX scramble was held on Sunday 19th and over 19 stations participated. Rod 3ZIW drew in the city section with George 3ZQJ, both with 26 points, while Bill 3ZLO took 25 points. In the country section, try section, with 23 points, followed by Graham 3ZIX/P with 19 points.

Try 3ZPC received a letter from Vern ZLAAQ confirming that it was his signals that were at R5 50 in Melbourne on 17th January, 1963.

The frequency of 144.5 Mc. was chosen some time ago and several people have been active on net frequency, but very few Amateurs seem to be using it. A small net sometimes gathers on a Monday evening at 8 p.m., but that is about all. There are numerous advantages for all stations active on 8 mX to be able to transmit on the one frequency. Originally the idea was to leave your group on 144.5 Mc. while you were working around the shack so that when someone called CQ they would do so on the net frequency and you would hear him without having to continually tune the band. Once contact was established the stations could then change frequency if they so desired. However, there is no reason why the contact should not stay on 144.5 Mc. with other stations joining in to form a net. Naturally by being able to transmit on the net frequency you could break in at any time. Those of you who do not possess a v.f.o. should try and get a crystal on the net frequency.

The annual general elections will have taken place by the time you read these notes and a new publicity officer will have been chosen. Thanks to Roy 3ZU for one year, a group who provided me with news during my brief fill-in period in the job. I hope to goodness the new officer receives much more assistance. Remember, the notes can only be as good as you care to make them. TZ, 3ARZ.

## SOUTH AUSTRALIA

50 Mc.: The 6 mX band has been showing the slight decrease in activity that we expect just after the sporadic E peak. DX was working on 50 Mc. from 10.15 to 11.15 on 19th and 11th (VK4s) on all three occasions.

Mobile has shown an increase recently, with 3ZDZ and 5LA having mobiles going and both being active on 50 Mc. There is also a cross-band duplex mobile, a very interesting exercise. Other new mobiles include Bar 5GZ and Curi 5CL (formerly 5ZBL). Mobiles are being used more and more by the conductor. These chaps will use 5GZAs and 5LSs respectively.

New to the 6 mX include Mark 5ZEK (50.4 Mc.) and Bob 5RF (a pair of 834s, wow!), Bob is at Murray Bridge (about 30 miles East of Adelaide) and puts a good signal into the city. Wally 5ZEH (50.11) is another newcomer.

Old timers on 6 mX from new locations are manifold, and include Doug 8SKK (also on the i.f. bands), Barry 5ZDI (These two in Darwin), also Brian 5ZBI, now at Clare (30 miles North), Brian looks on 6 mX every evening at 1800 (C.S.T.) with the beam towards Adelaide. Clare is only 50 miles away, but the path is very difficult. Joe 5ZCP, now at Whyalla, has been working back into Adelaide nicely (140 miles).

The 50 Mc. beacon has been running almost continuously over the past six weeks and ground wave reports are coming in from Mt. Gambier (220 miles), Western Victoria (180 miles), Crystal Brook (100 miles) and Yorke Peninsula (50 miles).

144 Mc.: Quite a high level of activity here. Several new country stations have helped the activity including 5ZGZ and 5ZMJ of Port Pirie (and both members of the newly formed Port Pirie Amateur Radio Club) and Geoff 5ZCG of Broken Hill. All these chaps have worked into Adelaide with excellent signals.

Rick 5EB is a new local on 144 Mc. He is located at Glen Osmond and uses an 832A. The chaps down at Mt. Gambier inform me that 5ZNR is often copied (three nights in one week recently). This smacks of duetting and the chaps are keen to try 288 and possibly 144 Mc. to the Apple tree, but no shad, have been organised since the date of writing. These same Mt. Gambier fellows say that our new beacon is heard down to a high percentage of the time (20% miles).

Eric 5ZDQ is building gear for 2 mX. Two metre stalwarts, 5NW (Crystal Brook) and 5EBC (Renmark), have been making good their 6 mX facilities recently, peaking many long distance (120 miles) duplex contacts between 6 and 2 mX.

General News: Biggest news the V.H.F. Group held on 4th March. New officers elected are: President, Doug 8SKK; Vice-President, Gary 5ZBK; Secretary, Alan 5ZGZ; Treasurer, 5ZCR and Brian 5ZBR. Discussed at the meeting were, firstly, a hidden tx hunt (first in VK8) to be held on 27th April, and secondly a v.f.o. hunt on 18th March.

Recent visitors to our fair State were Ken 3ZKK and Peter 3ZGM. These chaps had mobile gear on 6 and were worked at speed. Gary 5ZGR and Dale 5ZL are Mt. Gambier chaps who have been holidaying in Adelaide. Dale is well and truly involved in woman trouble, but Gary is more or less active, and, in fact, attended the V.H.F. Group meeting on 4th March.

Our newly elected President, Doug 8SKK, returns to VK5 in April. For their services over the past year the V.H.F. Group's President Gary 5ZK and ex-Secretary Barry 5BQ TZ, Al 5ZCR.

## WESTERN AUSTRALIA

Because of personal commitments, the notes for last month had to be shelved. I will attempt to cover them this month.

The January meeting was well attended and as reported in the first note for two months to discuss and act on items of business. John 6JO gave the lecture on xtal filters, clearing up a lot of doubts and giving us of us an insight into their operation and uses. A report was received on the very interesting fox hunt conducted by 6RY, using a different search method to determine the winner.

To start you took a mileage reading and filled in a form which was completed and handed in after you found the tx. You counted each mile and the number of times you used the converter/receiver and snook loop and subtracted these from 100. You subtracted 1 point for each mile and 1 point for each time you used the snook loop. You added points for the number of people in the car, the number of people who saw the tx and the number of people who found it. At the end of the latter, there was a tx and three antennae which could be switched and had quite a few txs and antennas going in circles as they appeared to come from different directions just as you seemed to have it pin-pointed.

The February meeting was well attended, although the D.C.A. trainees, who are part of the backbone of the Group, are still in

the field training. Two new members were welcomed to the Group, Jim 6RU and Harry 6EBZ are well known to most members. The Feb. fox hunt was run by Bob 6BE and as usual was quite interesting. Lance and Gill won the event and will run the next hunt on 18th March.

The Group station 6VF operated in the National Field Day on 80, 40, 20, 15, 10, 6, 2 and 14 metres. It is a pity that there was no 1 mX gear available as it would have been a clean sweep from 3.5 to 576 Mc. Kevin 6CZB again supplied his caravan and gear. Jim 6RU, Jack 6BU, Rod 6ZDS and Charles 6LK supplied other gear. David 6DI, Ken 6ZPF and the others of the Field Day Committee did a good job and all in all a good time was experienced by those who participated.

50 Mc. has been very quiet here for the last two months. Quite a few of the stalwarts are D.C.A. trainees and have been to country centres for the field training. The W.I.A. news was relayed on 6 mX for the first time in years and favorable comments were received after the broadcast. Vic 6VK has taken over from Wally 6WG as broadcast officer, following Wally retiring from this position, and he has arranged for Bob 6BE to relay the news on 6 mX. Best of luck to Vic and he can be sure of the backing of the group in his new post.

144 Mc.: Except for cross band work, this band is almost dead here, very few contacts have been heard for some time.

576 Mc.: Rod 6ZDS and Charles 6LK have succeeded in working a distance of 37 miles from North Dandelup to South Perth. Both rigs were xtal locked and are reported to be working extremely well. This contact was very close to a new 576 Mc. record and I believe it will be claimed as one. TZ, Allyn 6ZDM.

## PAPUA

50 Mc.: VK4s were worked on 2nd, 4th and 13th Feb. Also heard on these days were VK1, 1, 3 and 5. Weak ZLs were heard on the 4th and the 13th, a sound carrier was also audible during all three openings. No other DX openings were observed during the month. With the decline of the SE season, fewer Channel 2 openings were observed, however ABQ2 was received on 10 occasions, AB2S and AB2N each on one occasion.

9AS has returned from leave and is active again from Wewak, New Guinea. 8ZBV has now gone south on leave and will be having evelall 8Q80s with many Brisbane operators during the next month or so.

No activity on other bands during the month. TZ, Roy 9AU.



## DX NOTES

(Continued from Page 23)

The next few years, the following award might include VKs. Sponsor is 5L3ZO and his title is 80 x 80 Award. It comes in three classes: (i) 80 different countries on 80 mX. (ii) 80 different prefixes. (iii) 80 QSLs from stations outside one's own continent. Apply to Sven Elfving 5L3ZO, Solgardsgat 13, Ornskoldsvik, Sweden. Those holding Russian Call Books can write Sven at the above address.

## APPRECIATION

Let me thank again all those who have tried their best within their abilities and the trouble to send in what information they have. Those who appear in the activity section usually help out considerably with the QTH situation. Thanks to:

My appreciation also to the overseas editors K5CQV, WA6TGY, G2BVN, 5L3ZO, OH2TV, W2CDE, ON4MC and others who remember this column each month. TZ, Al, VK4SS.

## W.I.A. LOG BOOKS

5/6 plus postage





# FEDERAL AND DIVISIONAL MONTHLY NEWS REPORTS

(SEND CORRESPONDENCE DIRECT TO DIVISIONAL REPORTER NAMED AT PARA. END)

## FEDERAL

### 27th FEDERAL CONVENTION

The Wireless Institute of Australia's 27th Federal Convention will be held during 12th to 15th April, 1963, at Sydney.

The Convention will be held at the Wireless Institute Centre, 14 Atchison Street, Crosses Street, Headquarters of the VK2JW Division, W.L.A. The Convention will commence at 2 p.m. on 12th April and continue until 15th April.

On 13th April the Convention Dinner will be at the Wentworth Hotel, Lang Street, Sydney, at 7.30 p.m.

Opening of Convention will be broadcast over VK2JW on 7050 Kc. at 2 p.m. on 12/4/63, also a portion of the VK2JW Broadcast on 14/4/63 will be from the Convention.

All members of the W.I.A. will be welcomed.

Pierce Healy, VK4AR, Federal Councillor, N.S.W. Division.

### MATTERS OF INTEREST FROM W.I.A.

#### F.E. MEETINGS

Copies of some R.S.G.B. publications will become available at reasonable prices in the near future. Details from your Divisional Secretary.

All outstanding awards and certificates have cleared up and the appointment of a Federal Contest Co-ordinator within F.E. This has solved the difficulties involved with changes of locale of the F.C.C., often causing records of outstanding awards to become mislaid, or forgotten.

The Federal President will be attending the Civil Defence course at Mt. Macedon next year.

The subject of s.s.b. power ratings has been under study and this, and other matters, will be the subject of discussions with the F.M.G. in the near future.

The Federal Convention, which is to be held in Sydney at Easter, will cover some twenty agenda items.

New W.I.A. membership certificates are expected to be available by the time of publication. There is a very fine document of professional quality.

The Federal Station, VK3WIA, is near completion, and should soon be on the air regularly.

In order to ensure that no gaps exist in Federal Councillor's files, they are to be supplied with an index of all items discussed at Federal Conventions since 1947. This will help to avoid the same matters being decided over and over again over the years, as a study of past Conventions will show has happened.

Publication of the "Geneva Story" has been deferred until such time as the necessary attention can be cut by F.E. members. The reason for this is that commercially produced copies would cost in excess of £10 each in the small quantity required, and it is not felt that this expense would be justified, in view of the limited appeal that this publication has.

### RECIPROCAL AWARD JUDGING

#### WITH R.S.G.B.

The steady increase of postal costs, and the danger of valuable cards being lost, has long discouraged Amateurs from applying for overseas awards.

Now the R.S.G.B. has decided that its awards will be available on submission of certified check lists via certain I.A.R.U. Societies, or by the W.I.A. in one which have concluded reciprocal agreements with it. Such an agreement has been concluded with the W.I.A.

All R.S.G.B. certificates, with the exception of the Empire DX Certificate, and Four Metals and Down awards, but including B.E.R.T.A. (Commonwealth countries), W.B.E. (Commonwealth country in each of the five con-

## SILENT KEY

It is with deep regret that we record the passing of—

VK3WA—John H. Worner.

tinents), and for s.w.i.'s the H.B.E. award (heard 50 commonwealth countries) and the D.X.L.C.A. (heard 100 countries) are available and the procedure to apply is to send to the Federal Awards Manager, C/o. Box 2611W, G.P.O., Melbourne, the following:

(a) The necessary QSL cards.

(b) A check list, showing details of cards submitted.

(c) A declaration and application for award as follows:

I enclose cards herewith in my application for the R.S.G.B. (name of the award). I enclose International Money Order for 8/9 (Australian) for each certificate applied for.

I certify I have not exceeded my licensed power in effecting the contacts on which this claim is based.

Signed \_\_\_\_\_ Call Sign \_\_\_\_\_

A space must be left for the endorsement of the Federal Awards Manager.

(d) Sufficient return postage for the cards.

On receipt of the preceding, the Federal Awards Manager will verify the application and forward it to the G.S.B., who will forward the certificate direct to the applicant.

## NEW SOUTH WALES

### HUNTER BRANCH

The Feb. meeting of the Branch was held as usual in the University College, but in a different location in the building. For those who know what it is like within the confines of this edifice, the semicircular building, so called, is easy navigation. But for those unaccustomed it is like climbing a convex hill, you can always see the top but you never get there. After the usual "I am here" thirty-six in all, to see and hear some films kindly supplied by Mullard. These were expertly presented by Mr. S.C.C. Jones. He was ably assisted by Kev ZKXW. Always keen to keep us abreast of modern developments in electronics, Stuart ZAYF handed out some information concerning the new modulation and there was, on the board, a circuit of an overtone oscillator for v.h.f.

Some discussion ensued concerning the merits or otherwise of an f.f. choke, but it was kindly pointed out by Gordon Z2SG that OT's know nothing about v.h.f. and should stick to the d.c. bands. A rather academic discussion concerning the detonation of explosive charges by Amateur Radio transmitters was resolved by Frank Z4PO who is an army man and well versed in the science of loud and soft bangs. However it was decided that it would be a good scheme to get some official advice on the responsibility of the Amateur in such matters and by this time advice has no doubt been received.

Your scribbles have been responsible for the broadcasts during the past few weeks and Max, our associate friend from out Toronto way has been helping out in reading the news. The problem is whether to have a news item, a news producer or technical co-ordinator. I think the best term would be "the lad". Bill ZXT, who is equipped with much exotic gear now owns a very shiny new SX115 all the way from the U.S.A. He has proved that (a) WWV does not drift (b) the new rx does not drift, or (c) that he can also make a RA and in the same direction at the same time, etc., etc. Still he finds it difficult to copy me. Perhaps it is my signal.

Up by the banks of the old Hunter at Maitland Kev ZKXW is currently working on the "Mighty Midget" reputed to be some mysterious form of tuned converter for v.h.f. Some have suggested that he has also made a RA and future efforts in this direction will decide the issue. Mac Z2MO now is affectionately known by his mates as "Eddy". This has nothing to do with losses in his transformer. It refers rather to a gain in the rx department. Bob Z4QR has a weak signal out by the lake at the present time and it is because he is using all his energy to wind the movie camera for the filming of the F.F.B.R. (Fabulous Phenomenal Relay Rally) run by his partner in 40 m.c. crime, Bill Z2L.

John Z2JG is still delving among the mysteries of the one-eyed monsters and surely must be a specialist by now. And while on the subject of specialities, Des Z2DN is surely a contender for the title of master of v.h.f. since the construction of his mobile 100 Mc. If you would like to share in his enthusiasm come along to the April meeting and hear Des describe the rig. The battle of the 5 meters is still going on, but it is not in all areas of the Branch. Ian Z2IF is still not quite sure whether a decrease from 25 to 1/8 watt really causes an increase of two 5 points and Bill Z2ZK was heard giving a signal report the other night in this way: "You are strength 6 old man. Actually my meter reads 9 plus 10 db, but that's still 56 as far as I'm concerned." Bill also has a new vertical aerial. It really is something—a piece of wire tied in the tree at the back of the shack.

As for Les ZBJ, it is a shame that potent 1/8 watt and he is currently doing modifications to increase something—probably Ian's 5 meter reading. I am sorry to report that Neil Z2CU is still in Hornsby Hospital and would appreciate any visitors. VK2 Colossal Signals, as he calls himself, is almost ready to set sail for the land and sea boards and brown ale and leaving aboard a fine English ship at the end of April. So by sunny July in 12 days he should be on each side with some of the chums. Stan Z4YV is back from that Gold Coast holiday and is very active on 2 but not so much on 10. The old 529 group is better than the most recent one. Still no sounds have been heard from Norm Z2NF and if it were winter we might be excused for not being so busy. But it's all too hot here. But it's all too do with that AMR300 were told. Les Z4OR is not quite sure where Norm lives, but he has heard him say "I am here" and you'll see Norm. One of the boys in the mail room started shouting to Les the other day. When he asked what it was all about, the other chap said, "You are shouting for hearing aid on mate." What really happened was that he'd been listening to the test on the transmitter.

Bill Z2WM has two converters going now, one on 2 m.x and one on 40 m.x. The one he has on 2 m.x will be the subject of a lecture to be given at the next meeting. It really works well into a transistor portable. Since Tony Z2CT became a tuner of Yiddish pianos (he has been heard of him on 2 or any other metres).

Some of our younger members are trying out for the youth radio scheme certificates and the other day two were scheduled to turn up at this QTH for the junior exam. One however failed to report. Yes, it was Bill Z2L who had been held up when one of the pylons on the F.B.R. collapsed. Shame on you. You'll not get your certificate. Stuart Z4YF has gone all commercial you know. I saw responsible on his other side. He has got a s.w.r. meter and a transistor power supply transformer. Well, I ask you. Still he will be 2 and 40 mobile when the vacation begins and with home-brew gear. You might also know that he and I featured in the Newcastle Morning Herald the other day. Facts are that there was a Civil Defence conference and some person looked the front door of the building. Some, it said, had climbed over the back fence. Yes they were—us.

### N.S.W. DIVISION, W.I.A.

#### NTH. COAST & TABLELANDS

## ZONE CONVENTION

will be held at

URUNGA

during Easter Week-End

12th to 15th APRIL, 1963

144 Mc. tx hunt, 40 m.x tx hunt, all band scramble, general entertainment. Accommodation of all types available on application to Mr. J. Walters, C/o, Ocean View Hotel, Urunga.



# ADCOLA

(Regd Trade Mark)

## SOLDERING TOOLS

This range of precision made soldering tools and equipment, widely used overseas, has been designed and developed to facilitate the fastest and most efficient soldering of standard and miniaturised radio and electronic equipment.

### Approved Mains Voltage Tools:

- No Transformer required. Supplied for all voltage ranges from 6/7V. to 230/250V.
- Instant CORRECT Temperature.
- Light weight, perfect balance.
- Low Loading, and cheap to operate.
- Long life.

Further information from Manufacturers:-


**ADCOLA PRODUCTS**  
PTY. LTD.

673 WHITEHORSE ROAD, MONT ALBERT, VIC.

Telephone 88-4351. And all principle radio parts supply houses.



**CHOOSE THE BEST—IT COSTS NO MORE**

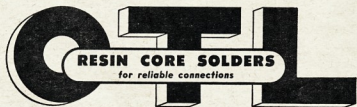

G. T. LEMPRIERE & CO. LIMITED. Head Office: 27-41 Bowden Street, Alexandria, N.S.W.  
and at Melbourne • Brisbane • Adelaide • Perth

room does not lend itself to such goings on with Ham equipment. All is not lost, however, as 80 mx mobile is in course of construction and will soon burst gloriously forth if the jalopy is strong enough to pull it.

Where are our long lost sons, Gordon 3GW and Keith 3QG, who so nobly offered to work us from the State capital where they now reside? Let us not lose heart, though, for Max 3AR is nearly ready for the hook-up with his first home-brew gear and Mac 3AZM has moved into Horsesham and looks like being a regular on the weekly net.

We have missed Herb 3NN for a long time now but as son Gary has obtained a Limited licence there should be at least one, if not two, signals from Yanac shortly.

Bert 3EF still radiates steadily on at Warracknabeel, sometimes 80, sometimes 40, sometimes DX, but always with a signal to be proud of—or should it read "of which to be proud". Well, fellows, you asked for it—putting this month's compilation in dubious hands. Cheers, Vic 3AEQ.

### EASTERN ZONE

The Eastern Zone will hold their annual Convention during the week-end April 20 and 21, 1963, at Warragul. Full details will be on the invitation cards which you will receive shortly. Welcome to any visitors.

A Zone meeting took place on Sunday afternoon, Feb. 17, in Bert's (3HH) back garden. The main items discussed were the coming Convention, initial arrangements for the Zone W.I.C.E.N. Gippsland Control Centre and Network.

Also keeping activity high in the Zone (and in view of the coming W.I.C.E.N. network) it has been decided to hold the Eastern Zone hook-up now at 2000 hours on Sunday evening on 3650 kc. approx. and 144.18 Mc. What about joining in everyone? This should be a much more convenient time for everybody. See you all at the Convention. 73, 3ZCG.

### QUEENSLAND

February always leaves me with a feeling that I've been "got at". The end of the month sneaks up and March is well started, by the time I wake up that I'm a few days short. My spies in Brisbane apparently suffer from the same trouble or else they are all living very pure lives. Well, nearly all.

The "Kingsfisher" group, which meet regularly at 0900 each day on 40 mx, decided to get together on a "Hamboree". That will stop Mr. Webster, because he doesn't even list "Jamboree" in his famous book. Anyway, Sunday, 24th Feb., was the date selected for the first "Kingsfisher Hamboree". It was held at Caves Creek in the glorious setting of the Numinah Valley.

After their usual morning "sked", the group headed for the Hamboree. Alf 4OL, being a good scout, is always prepared, and used his mobile to good effect, telling various VK2s about the proposed outing. When he arrived at the spot selected, he found Jeff 4XP, George 4GG and Tom 4PD heading out of the area in search of firewood, and being QSO with 2CH at the time, the make was passed between cars so as to enable said wood gatherers to say hullo to 2CH. What some blokes will stoop to do, to get out of chopping wood. When I was younger and used to go on picnics, always . . . Never mind, you wouldn't believe me anyway.

During the afternoon, the "Hamboree Cake" was unveiled and George 4GG, armed with an axe, cut it. And what's more, got his photo "took" whilst doing it. I'm sure Mavis, his YF, smartly put him in the doghouse for that. Mavis, by the way, made the cake and I'm told it was very beautifully iced. I'll bet George was too, after his effort with the axe. I have no sympathy for you George. To play a trick like that on your YF. Shame on you. And to think that he gets a cuppa in the morning, his slippers brought to him, his licence paid, his log book kept up to date. How can you do it? Words fail me. Thanks Mavis, I would like a piece of that cake.

Jeff 4XP, Howard 4WO, Les 4EH and family, together with Bill 4ZBD and YF also attended the Hamboree. The only Kingsfisher absent was Bill 4WS, who was ill. A total of 29 attended the outing and general opinion was that it was a huge success and that it will probably end up as an annual event.


The Central Qld. Branch had their monthly meeting on 15th Feb. and it was very well attended. Their Patron, the Mayor, Alderman R. Philbeam, was also in attendance. Main business of the evening was election of officers for 1963. Frank 4FN was re-elected as President, Secretary is C. Bennett, Treasurer W. Peterson and Publicity Officer is 4ZCK. Frank 4FN sounded a warning to those not using







## UNIVERSAL SOUND

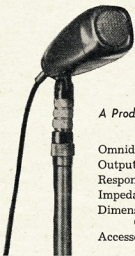

*A Product of Italy*

Omnidirectional.  
Output: —50 db.  
Response: 50-12,000 c.p.s.  
Impedance: 50,000 ohm, 250 ohm or 60 ohm.  
Dimensions overall: 40 x 40 x 98 mm.  
(1-9/16" x 1-9/16" x 3-13/16").  
Accessories: Table base.

### DYNAMIC MICROPHONE Model 603



Model 603 is a Dynamic Microphone ideal for music, speech and particularly magnetic recording. Can be used on stand or on a small table base.

Smart square shaped aluminium pressure cast case with stainless steel wire mesh.

Sturdily built and beautifully finished. Impedance can be easily stepped down from high (50,000 ohm) to low (60 or 250 ohm) impedance.

Retail Price: £14/0/0  
Plus Sales Tax £1/9/2

Marketed by **ZEPHYR PRODUCTS PTY. LTD.**

58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

Phones: 25-1300, 25-4556

## STEP-DOWN TRANSFORMERS

*for a host of applications!*



RADIO



TAPE RECORDERS



SHAVERS



HEATING BLANKETS

PROJECTORS



The newest and latest addition to the already comprehensive range of A & R Transformers. Data sheets listing all types are now available from "The Transformer People."

Send for Specification Sheet and Price List NOW!



TV PICTURE TUBE BOOSTERS



VALVE FILAMENTS & HEATERS



SOLDERING IRONS



BATTERY CHARGERS



PILOT & SAFETY LIGHTS

**A & R ELECTRONIC EQUIPMENT CO.**

PTY. LTD.

46 LEXTON RD., BOX HILL, E.11, VIC. P.O. BOX 9

POST THIS COUPON

NAME.....

ADDRESS..... STATE.....





month I paid my Radio Amateur licence at the Norwood Post Office instead of tracking all the way up to the Receiver of Public Monies at the G.P.O. This will bring joy to Max 2ARZ, to several boys in VK4, and to several of the VK3 fraternity, who have never let the matter die since my original paragraph two or three years ago. Oh dear, oh dear, however will I fill these notes now? Don't answer that.

One of the members rushed up to me at the meeting and said in a very threatening manner, "A bloke from Eyre is going to have a go at you, sense of propriety will not be offended nor will you have to read my mutilation of the English language. There is no truth in the rumour that I am feeling the State because in my description of the "Kmas Doo" I was foolish enough to say of the three charming young ladies in the kitchen—"May they shadow the night less. Woe is me! T3 de SPS—PanSy to you."

Well, here we are again, annual leave time. The notes next month will be written by that ace journalist, Brian SCA, I hope, and for once your sense of propriety will not be offended nor will you have to read my mutilation of the English language. There is no truth in the rumour that I am feeling the State because in my description of the "Kmas Doo" I was foolish enough to say of the three charming young ladies in the kitchen—"May they shadow the night less. Woe is me! T3 de SPS—PanSy to you."

— . . . —

## WESTERN AUSTRALIA

**Pow! Pow!** Two shots rang out and Paladin lay writhing in the blood-soaked dust, heels kicking spasmodically, while Ross Bonanza stared at him through slitted merciless eyes over the top of the smoking, hammerless revolver—oh! What's the time? What band are we working? What? It can't be March! It's April! Heck! Next it'll be Easter time, the end of the financial year! Here it is half the year gone and nothing done. So get with it, chaps!

Talking about doing something, had a personal contact with Pat 6PH recently, and discussion got round to the psycho tests given to a candidate for the Armed Services. The old one was mentioned and Pat said they really did see a ship in the middle of the jungle up in the islands. It had apparently sailed there some time ago, but in the winter season and got stuck and there the corvette was, viewed with some surprise by Pat and the mob. Well? What about you old Yeppies? I'll bet there wasn't any radio gear left on it by the time Pat had passed by.

Mention of Radio gear reminds me, our Technical Officer, RALPH 2EAD, is waiting on the Divisional B342 Rx so that it will be in tip-top shape for use by our new Broadcast Officer, Vic 6VK. Good work, Ralph, don't spare the expense, but the tx another valve. Congrats, too, to Vic as Broadcast Officer. Vic says the W.A. news will be broadcast

**Repairs to Receivers, Transmitters; Construction and Testing; T.V. Alignment; Low Noise Xtal Conv., any frequency, £18/10/0 plus tax.**

## ECCLESTON ELECTRONICS

146a Cotham Road, Kew, Vic. W9 3777.

## D.C. CONVERTER TRANSFORMERS

Miniature toroidal transformers for transistor d.c. to d.c. converters. Fully encapsulated in epoxy resin. Suitable for horizontal or upright mounting. Voltage doubler circuit.

12v. in, 300v. 100 mA. out . . . . . £4  
12v. in, 300v. 200 mA. out . . . . . £5

Other voltages up to 350 watts output supplied to order.

400v. silicon rectifiers . . . . . 8/11

Above prices subject to sales tax. Carriage free.

## ELIZABETH ELECTRONICS

P.O. Box 7, Elizabeth, South Aus.

simultaneously on 80 (s.s.b.) and 40 (a.m.) and re-broadcast on 6 m by Bob 6BE. In handing out the bouquets, I was very glad to see who carried the news broadcast for so many years. This wasn't the only job Wal was doing of course, he is still membership secretary, cheerleader, and thanks to me for all a fine job.

A fine job calls to mind that the v.h.t. boys have been doing a splendid job of running the service for car trials seems to be a regular thing nowadays, and, I would suggest, an excellent stimulus for getting Hams operating mobile. Enthusiasm evident in large lumps everywhere. That reminds me, what happened to that vibrator power supply I loaned someone for the first car trial? Mum!

Alyn 6ZDM tells me he wants someone to develop a new device. This is called a "clot" suppressor. Specifications: 1. It should be entirely automatic once the rx is tuned in, be able to discriminate between clots and non-clots, have a bandwidth of 15 cycles to 15 kc. a.m., l.m., and s.b., with the ability to turn the far end tx off after a reasonable time as a desirable characteristic.

Our President (Ron 6KW) having recovered from the slight loss of his left eye, his eyes normal shape and has stopped drinking salt, turned the tx key on recently (no squeaks) and got himself 63 on 21 megs. Ron says he's having a great trouble, and that all the hyphens getting stuck Ron, and making the wind brittle. Oddly enough, Allen 6WQ doesn't even want the VQI. Perhaps that's quads' not quite cubical or something. Allen.

Have a couple of sickies on the list at the moment. Associate Ross Hardwicke not enjoying the best of health at the time of writing, so we trust that all is OK again by the time you read this. Same Assoc. who will make the February meeting either, because he had an argument with a car, whilst he was on the pedestrian path of the footway. Geo. was able to go home after observation at the hospital. Hope there are no after effects Geo, and you are about for the next meeting.

Believe it or not, the 6PH and 6GP trip into the Great Southern recently, were through Bunbury at a rate of knots so did not see the 6WL or Cole 6GL (incidentally, if you see the mole on the price of the amber fluid) and raced on to Katanning to join the X Group in the congenial surroundings of the Katanning Club. Geo. certainly appears to be enjoying his retirement. A fine figure of a man. A gentleman and a scholar, sir. Besides, he knows a thing or two about radio. He knows a thing or two about technical articles we get after the news broadcasts on Sundays. Keep it up, Geo., they're regular.

The real news I have from the country this month is word of 6LF racing down from Carnarvon to Geraldton recently to be in the local paper. Gee! Did you follow the signal all the way!

As regards the State generally, Tony 6TV, who labours for the D.C.A., says there are two of every conceivable piece of radio gear in various parts of the country in preparation for the Royal visit, so we hope everything works OK.

Well, there it is, chaps, if you are shy about seeing your own name in print, put some of your coppers in and I'll mention them. Cheers for now, 6LS.

## TASMANIA

Our Divisional Council elections will be over by the time these notes are published, but I wish to publicly acknowledge our debt to two retiring Councillors, namely, Ken TKA and Allan VYK, both of whom are not seeking re-election. Ken TKA has been our Divisional Secretary for six years, during which time he has laboured long and well for us, and I am not aware of Ken having missed a Council meeting, and I am only aware of one Divisional general meeting being missed by Ken in all that time. At one time, Ken was our Secretary, Bulletin editor, publisher and distributor, and Sunday morning broadcast officer, all of which among other things, was a great job for one man. Mercifully, our next Secretary will not have to cope with all these duties. In addition to his other duties, Ken has been an active supporter of the various Divisional activities, including participation in the Remembrance Day Contests annually, the National Field Days, and other functions such as those sponsored by the Club Room Fund-Raising Committee. Ken, we understand your desire to relinquish the post of Secretary and we thank you sincerely for your many good works. Allan TMY has been a Councillor for two years on this occasion. Allan was responsible

for providing the technical article in our monthly Bulletin, and he has always taken a keen interest in the various technical activities, as well as being on more Amateur bands than any other Amateur in VK1. Allan re-transmits the official broadcast on the 6 and 2 m bands. He has done all this while building a new home and carrying on his livelihood as a farmer. We thank you also much, Allan, for your interest in the Division when Councillors were hard to get.

David TZAY celebrated his 21st birthday on 14th March, and while Dorothy TZAY reached the same age on 20th March, so congrats, to both of you chaps.

The VK7 participation in the National Field Day was a bit of a disappointment this year, but congrats to John 7ZF for his fine effort. Other stations heard by me were 7DK, 7CH, 7LJ, 7ZJ, 7ZL, 7ZM, and 7ZV. The 7ZJ, 7ZL, 7ZM, and 7ZV were very good during the A.R.R.I. Contest in Feb. were really excellent and many stations were worked by the few VK7 stations to take part. Conditions on the B.E.R.U. Contest, however, were not very encouraging, even though Pacific area stations at times were worked.

Our March lecture was on Tunnel Diodes, and what a truly excellent address this turned out to be. Not only was the theoretical side of the subject well covered, but the demonstration of gear was most impressive.

Anne Landers has recently taken delivery of her new 6AR5, and has been able to get proper functioning order very shortly. Members, remember that subscriptions are now overdue. Please forward your dues to Box 838, C.P.O., Hobart, now and save the Secretary the troubles connected with removing and re-instating your name on the circulation of this magazine.

The Youth Radio Clubs are now receiving concentrated attention from this Division. I have to thank ZYA for supplying me with all the necessary information on this topic. We now hope to proceed at a pace to have projects within this Division. If you can help with this project, let your Council or Zone Secretary know. We will be able to use your services.

We were delighted to meet Bob 4RW down to Hobart during the Divisional meeting. He was welcomed into many of our homes here and was also able to attend the meeting of the V.H.F. Group on 29th Feb. We hope to meet up with you on the bands. Bob 4RW, 7A, Jan TZZ.

## NORTH-WEST ZONE

The meeting in March was a social event with an enjoyable selection of movies by courtesy of Sid 7SF. Sid also gave us a work-out demonstration of a new 100 watt tx.

The evening was marred somewhat by a communication from the Southern Zone unequivocally advising of our status. It is most distressing that no diplomacy is not employed in such circumstances.

There seems to be little activity on the bands, although Ken TKA has been working some DX on 20. I noticed Winston has mobile whip on his car and 7ZBH is mobile on 14.

David TMS seems to have big things in mind and plans to surprise us with a new rig. I wonder if another "duck" is about to take to the air.

Had an interesting talk with visitor Bob 4RW recently. His zone in VK4 apparently has no duck, etc., or, curs, so the picture seems the same old picture.

The tx hunt on 17th March is now over, so no doubt the winner has been announced. 7Z, 7ZBH.

## HAMADS

Minimum 5/-, for thirty words. Extra words, 2d. each.

Advertisements under this heading will only be accepted from Institute Members who desire to dispose of equipment, which is their personal property. Copy must be received at P.O. Box 38, East Melbourne, C.S. Vic., by 8th of the month and retention should accompany the advertisement. Call signs are not permitted in Hamads. Dealers' advertisements not accepted in this column.

**SELL:** Heath DX40 complete, 144 Converter, Gelo V.f.o., 522 Xntr. Tubes and Xtal, RF26 Unit, Responder Unit, 108 Transceiver, Eddestone 750, excellent condition. VKAK, 72 Canning St., Warwick, Qld.



# WARBURTON FRANKI

for the exact model you want in

# MULTIMETERS

## SANWA-KAMODEN 370-NTR

### D.C. Volts:

0 to 100 mV., 2.5V., 10V., 25V., 100V., 250V. at 100,000 ohms per volt.

0 to 1 kV., 5kV. at 25,000 ohms per volt.

### A.C. Volts:

0 to 2.5V., 10V., 25V., 100V., 250V., 1 kV. at 10,000 o.p.v.

### D.C. Current:

0 to 10  $\mu$ A., 100  $\mu$ A., 1 mA., 10 mA., 100 mA., 1 A., 10 A.

### Resistance:

0 to 5K, 50K, 500K, 5 meg., 50 megohms.

Decibels: —20 to +62.

Size  $5\frac{1}{4}'' \times 7\frac{1}{4}'' \times 2\frac{1}{2}''$ . Weight 2 lb. 14 oz.

Price: £19/5/0 plus Sales Tax 12½%.

## T.M.K. TP55

### D.C. Volts:

0 to 10, 50, 250, 500, 1,000 at 20,000 o.p.v.

### A.C. Volts:

0 to 10, 50, 250, 500, 1,000 at 10,000 o.p.v.

### D.C. Current:

0 to 50  $\mu$ A., 0 to 5, 50, 500 mA.

### Resistance:

0 to 10, 100K, 1 meg., 10 megohms.

Decibels: —20 to +36 db.

Capacity: 50 pF. to 0.1  $\mu$ F.

Size  $3\frac{1}{2}'' \times 5\frac{1}{2}'' \times 1\frac{1}{2}''$ . Weight 13 ozs.

Price: £8/2/6 plus Sales Tax 12½%.

## UNIVERSITY MVA-3

### D.C. Volts:

0 to 10, 50, 250, 1,000 at 5,000 o.p.v.

### A.C. Volts:

0 to 10, 50, 250, 1,000.

### D.C. Current:

0 to 1, 10, 50, 250 mA., 10 Amps.

### A.C. Current:

0 to 1 mA.—use current transformer for A.C. Ampere ranges.

### Resistance:

0 to 1K, 10K, 100K, 1 megohm.

Size  $5\frac{1}{4}'' \times 8\frac{1}{4}'' \times 4\frac{1}{4}''$ . Weight 6½ lbs.

Price: £17/10/0 plus Sales Tax 12½%. Leather case available at £3 plus S.T.

## JEMCO MT955

### D.C. Volts:

0 to 2.5, 10, 50, 250, 1,000 at 50,000 ohms per volt.

### A.C. Volts:

0 to 2.5, 10, 50, 250, 1,000 at 5,000 ohms per volt.

### D.C. Current:

0 to 100  $\mu$ A., 10 mA., 100 mA., 500 mA., 10 Amps.

### Resistance:

0 to 20K, 200K, 2 meg., 20 megohms.

Decibels: —20 to +46 in five ranges (0 db. = 1 mW., 600 ohms)

Size  $5\frac{1}{4}'' \times 7'' \times 3''$ . Weight 2½ lbs.

Price: £18/18/8 plus Sales Tax 12½%.

## KEW TK70B

### D.C. Volts:

0 to 10, 50, 250, 1,000 at 20,000 o.p.v.

### A.C. Volts:

0 to 10, 50, 250, 1,000 at 9,000 o.p.v.

### D.C. Current:

0 to 500  $\mu$ A., 10 mA., 250 mA.

### Resistance:

0 to 20K, 200K, 2 megohms.

Size  $3\frac{1}{2}'' \times 5\frac{1}{2}'' \times 1\frac{1}{2}''$ . Weight 1 lb.

Price: £7/12/0 plus Sales Tax 12½%.

## AVO MULTIMINOR

### D.C. Volts:

0 to 100 mV., 2.5V., 10V., 25V., 100V., 250V., 1,000V. at 10,000 o.p.v.

### A.C. Volts:

0 to 10, 25, 100, 250, 1,000 at 1,000 o.p.v.

### D.C. Current:

0 to 100  $\mu$ A., 1 mA., 10 mA., 100 mA., 1 Amp.

### Resistance:

0 to 20K, 2 megohms.

Size  $3\frac{1}{2}'' \times 5\frac{1}{2}'' \times 1\frac{1}{2}''$ . Weight 1 lb.

Price £12 plus Sales Tax 12½%, including Leather Case.

## T.M.K. 500B

### D.C. Volts:

0 to 0.3, 1.2, 3, 12, 30, 120, 300, 600, 1,200 at 30,000 o.p.v.

### A.C. Volts:

0 to 0.3, 1.2, 3, 12, 30, 120, 300, 600, 1,200 at 13,000 o.p.v.

### D.C. Current:

0 to 0.06, 6, 60, 600 mA., 0 to 12 Amps.

### Resistance:

0 to 60K, 6 meg., 60 megohms.

Decibels: —20 to +57 db.

(0 db. = 1 mW., 600 ohms)

Shorts Test: Internal Buzzer.

Size 3-5/16" x 6-5/16" x 2-1/2"

Weight 1½ lbs.

Price: £13/15/0 plus Sales Tax 12½%.

## SAKURA TR6S

### D.C. Volts:

0 to 10, 50, 250, 500, 1,000 at 20,000 o.p.v.

### A.C. Volts:

0 to 10, 50, 250, 500, 1,000 at 10,000 o.p.v.

### D.C. Current:

0 to 50  $\mu$ A., 2.5 mA., 25 mA., 500 mA.

### Resistance:

0 to 5K, 50K, 500K, 5 megohms.

### Decibels:

—20 to +5 db. 0 to +22 db.

(0 db. = 0.775v., 600 ohms)

D.C. Volts range may be extended to 25,000 volts with an E.H.T. probe.

Size  $4\frac{1}{8}'' \times 6\frac{1}{4}'' \times 2\frac{3}{8}''$ . Weight 1 lb. 6 oz.

Price: £8/4/0 plus Sales Tax 12½%.

## 200H or ITI-2

### D.C. Volts:

0 to 5, 25, 50, 250, 500 and 2,500 at 20,000 o.p.v.

### A.C. Volts:

0 to 10, 50, 100, 500, 1,000 at 10,000 o.p.v.

### D.C. Current:

0 to 50  $\mu$ A., 2 mA., 5 mA., 250 mA.

### Resistance:

0 to 60K, 6 megohms.

### Capacity:

10 pF. to 0.1  $\mu$ F.

### Decibels:

—20 to +22 db.

Size  $3\frac{1}{4}'' \times 4\frac{1}{4}'' \times 1''$ . Weight 9 oz.

Price: £5/4/0 plus Sales Tax 12½%.



# WARBURTON FRANKI

359 LONSDALE ST., MELBOURNE — MU 8351




- TRADE ALSO SUPPLIED
- OPEN SAT. MORNING

Please include postage or freight with all orders.

# TRANSISTOR RADIOS

## Circuitry and Servicing

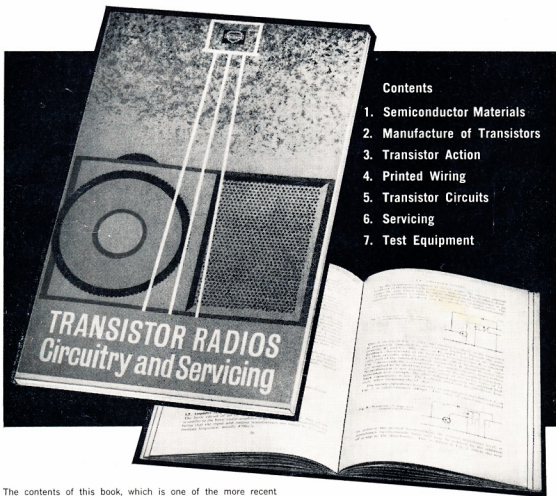

### Contents

1. Semiconductor Materials
2. Manufacture of Transistors
3. Transistor Action
4. Printed Wiring
5. Transistor Circuits
6. Servicing
7. Test Equipment

The contents of this book, which is one of the more recent Mullard publications, includes a simple explanation of the function of the transistor, the complex processes involved in transistor production, care and methods of repairing printed wiring boards, detailed descriptions of circuits likely to be encountered in transistor radios and the test equipment required.

Practical considerations are emphasised throughout the book, which is priced at 5/3, plus 8d. postage, and is available from most booksellers and from Mullard Offices and Distributors throughout the Commonwealth.



Mullard-Australia Pty. Ltd., Box 2118, G.P.O., Sydney

Please send me \_\_\_\_\_ copies of 'Transistor Radios Circuitry and Servicing' for which I enclose \_\_\_\_\_ remittance, being 5/3, plus 8d. postage per copy.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

STATE \_\_\_\_\_

MULLARD-AUSTRALIA PTY. LTD., 35-43 CLARENCE STREET, SYDNEY, 29 2006; 123 VICTORIA PARADE, COLLINGWOOD, N.S. VIC., 41 6644

Associated with MULLARD LIMITED, LONDON

M13